



McGill

Computer Organization

Processor Implementation


ECSE 324

Fall 2020

Prof. Christophe Dubach

The Processor

 - A processor is responsible for reading program instructions from the computer's memory and executing them.
- It *fetches* one instruction at a time.
- It *decodes* (interprets) the instruction.
- Then, it carries out the actions specified by the instruction



Die photo of an ARM Cortex-M3 processor



Processor building blocks

- PC holds the address of the next instruction to be fetched and executed


- Instruction is fetched into IR:

$$IR \leftarrow [PC]$$

- Instruction address generator updates PC (for straight line code):

$$PC \leftarrow PC + 4$$

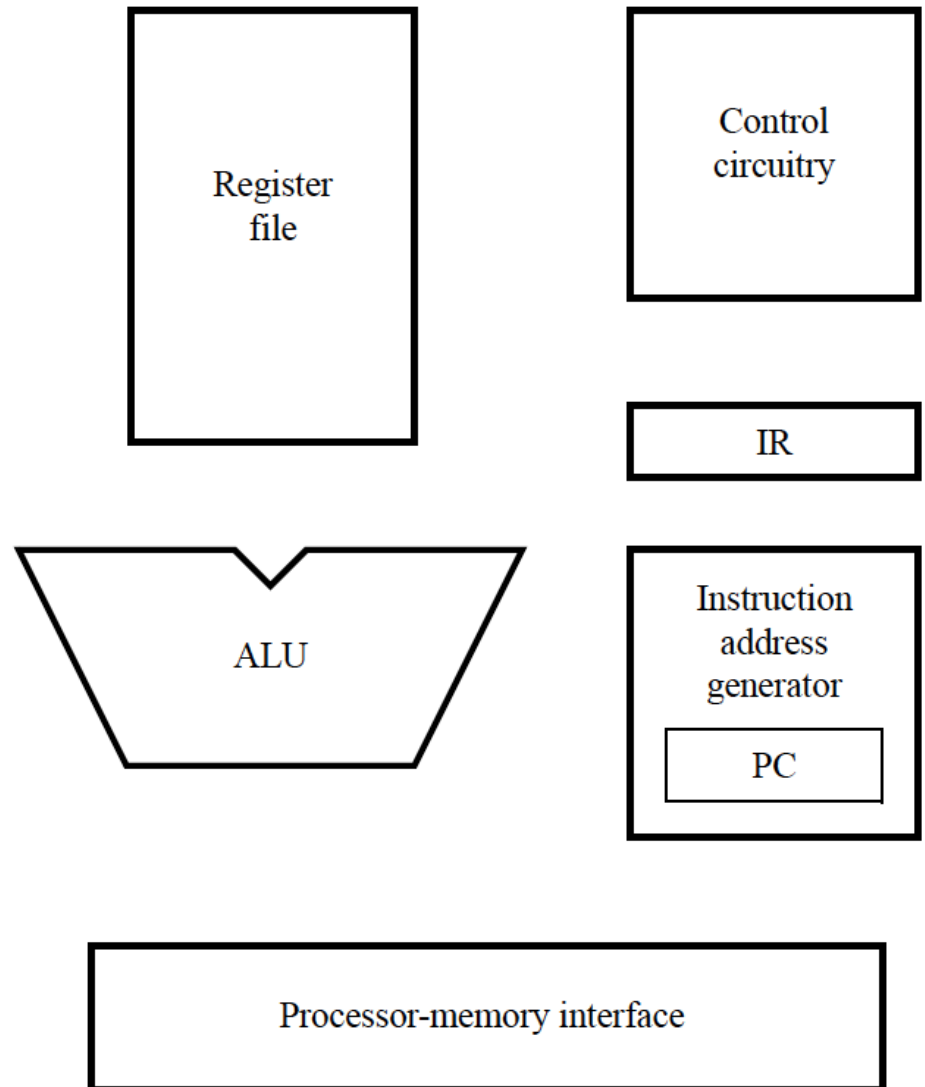- Control circuitry decodes the instruction and generates control signals that direct the datapath



Processor building blocks


- PC holds the address of the next instruction to be fetched and executed
- Instruction is fetched into IR:

$$IR \leftarrow [PC]$$

- Instruction address generator updates PC (for straight line code):

$$PC \leftarrow PC + 4$$

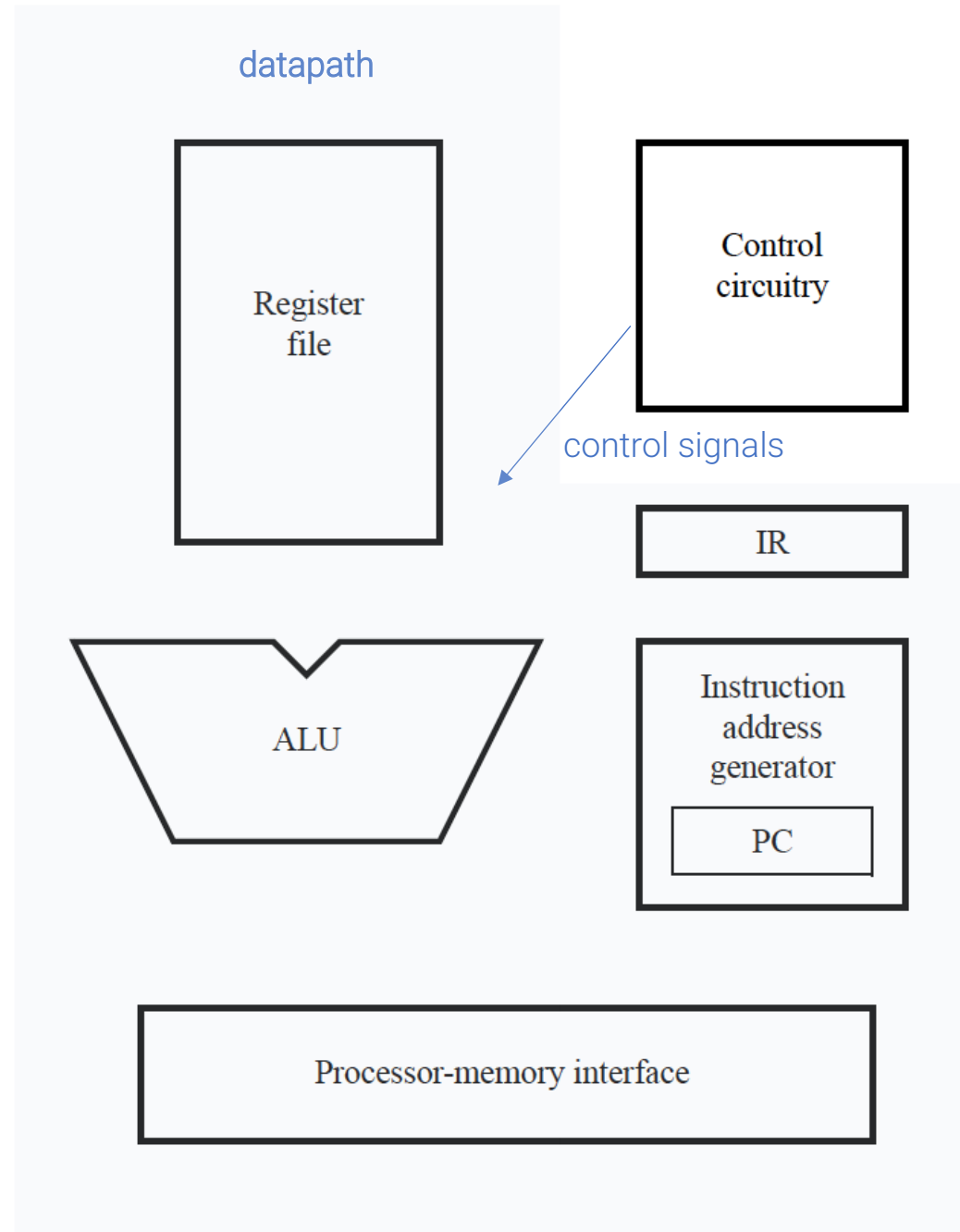
- Control circuitry decodes the instruction and generates control signals that direct the datapath



Datapath design


Textbook 5.1-5.4

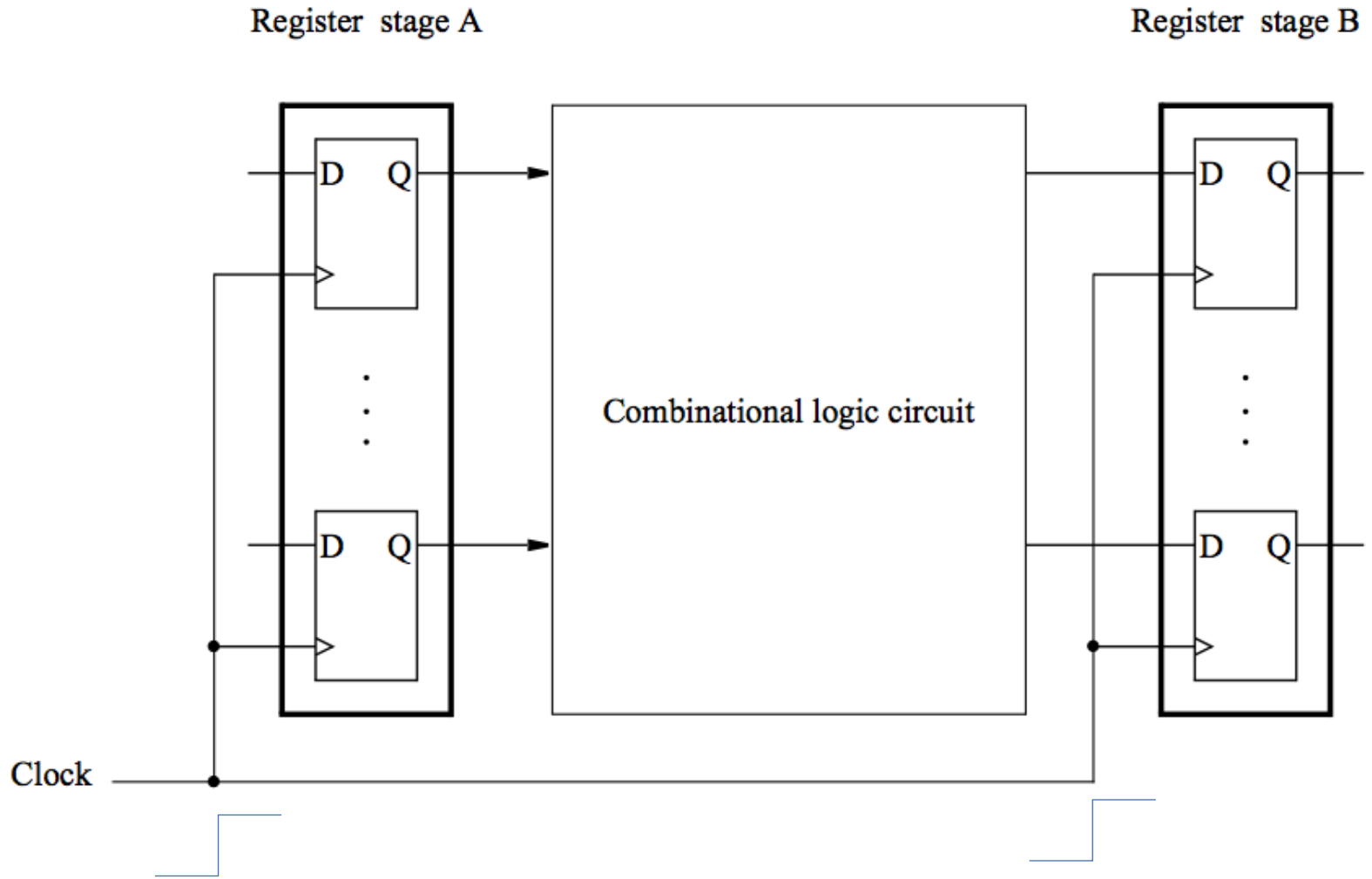- Contents of register A are processed and deposited in register B



clock period is determined by the delay of the combinational logic circuit

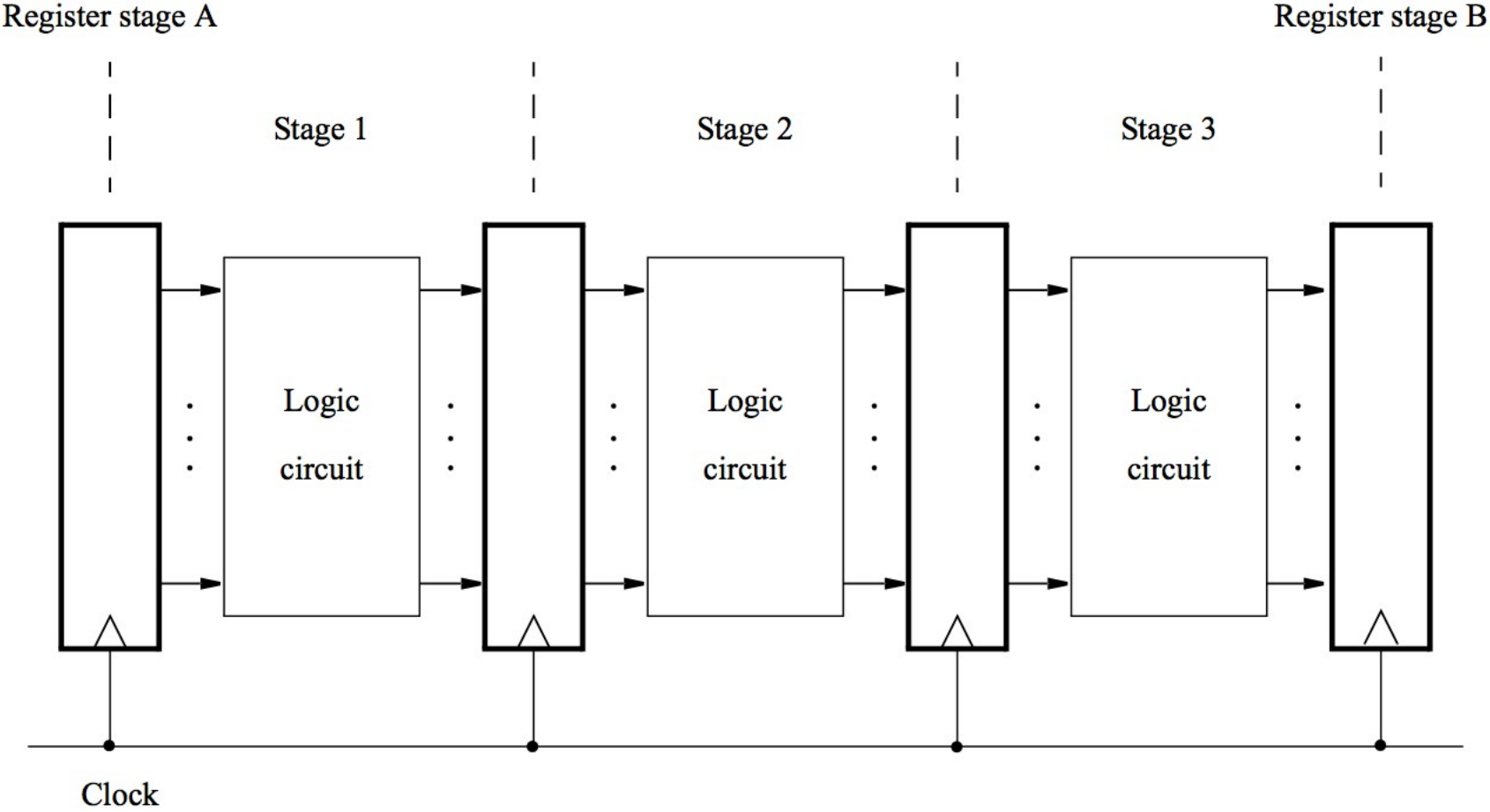- Combinational circuits can be divided into simpler subcircuits that are cascaded into a multi-stage structure.
 - n stages: n clock cycles to complete the operation
 - Clock period can be shorter: 1/n
 - Can be pipelined (overlap the execution of several instructions)



Instruction execution

- In RISC machines, all instructions are executed in the same number of steps.
- Each step is carried out in a separate hardware stage.
- RISC processor design will be illustrated using five hardware stages
- The processor design will model the basic RISC instructions and addressing modes, but not every detail of an ARM ISA

Load instruction

LDR R5, [R7, R8] R5 ← [R7 + R8]
 offset mode

1. **Fetch** the instruction and increment the program counter
2. **Decode** the instruction and read the contents of registers R7 and R8 in the register file
3. **Compute** the effective address $Z \leftarrow R7 + R8$
4. Read the **memory** source operand [Z]
5. **Write** the operand into the **destination register**

R5 ← [Z]

Arithmetic and logical instructions

Add R3, R4, R5 $R3 \leftarrow R4 + R5$

1. **Fetch** the instruction and increment the program counter
2. **Decode** the instruction and read registers R4 and R5 from the register file
3. **Compute** the sum $Z = R4 + R5$
4. No action why do we need this step ?
5. **Write** the result into the **destination register**

$R3 \leftarrow Z$

Stage 4 (memory access) is not involved in this instruction.

Immediate Operands

Add R3, R4, #1000 $R3 \leftarrow R4 + 1000$

The immediate operand is given in the instruction word and can be found in the IR.

1. **Fetch** the instruction and increment the program counter
2. **Decode** the instruction and read register R4 from the register file
3. **Compute** the sum $Z = R4 + 1000$
4. No action
5. **Write** the result into the **destination register**

$R3 \leftarrow Z$

Load instruction (immediate)

LDR R5, [R7, #X] $R5 \leftarrow [R7 + X]$

The immediate operand is given in the instruction word and can be found in the IR

1. **Fetch** the instruction and increment the program counter
2. **Decode** the instruction and read the contents of register R7 in the register file
3. **Compute** the effective address $Z \leftarrow R7 + X$
4. Read the **memory** source operand $[Z]$
5. **Write** the operand into the **destination register**

$R5 \leftarrow [Z]$

Store instruction

STR R6, [R8, #X] MEM[R8+X] ← [R6]

1. **Fetch** the instruction and increment the program counter
2. **Decode** the instruction and read the contents of registers R6 and R8 in the register file
3. **Compute** the effective address $Z = R8 + X$
4. Store the contents of register R6 into memory location $X + [R8]$ MEM[Z] ← R6
5. No action

Summary – Actions to implement an instruction

1. **Fetch** an instruction and increment the program counter.
2. **Decode** the instruction and read registers from the register file.
3. Perform an **ALU** operation.
4. Read or write **memory** data if the instruction involves a memory operand.
5. **Write** the result into the **destination register**


5 hardware stages will be needed

Stages 1, 2, and 3 will be used for all instructions

Stages 4 and 5 may not perform a useful action for some instructions


Hardware components: Register file

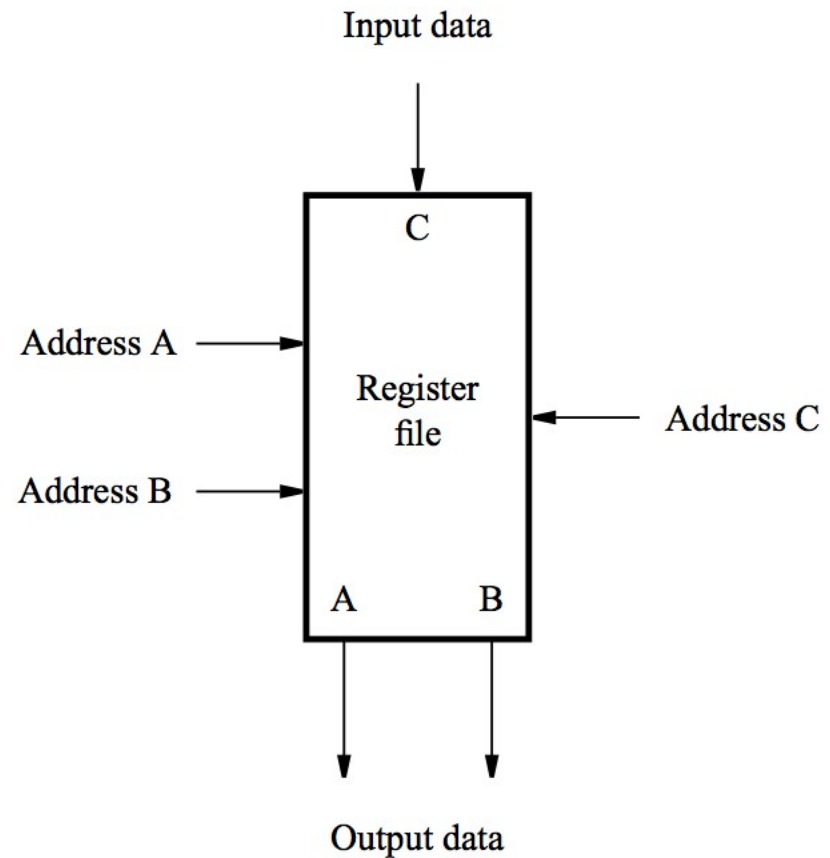- A 2-port register file is needed to read the two source registers at the same time.
- It may be implemented using a 2-port memory.




Alternative implementation of 2-port register file

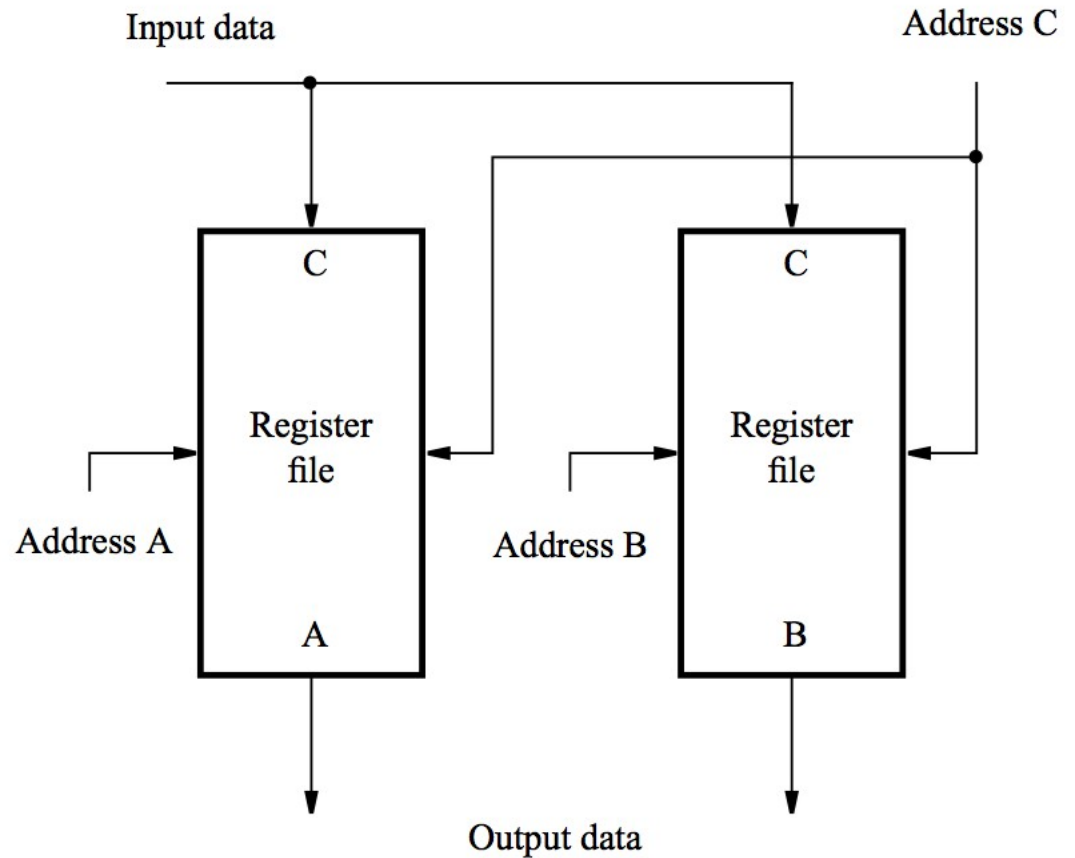- Using two single-ported memory blocks each containing a copy of the register file




ALU

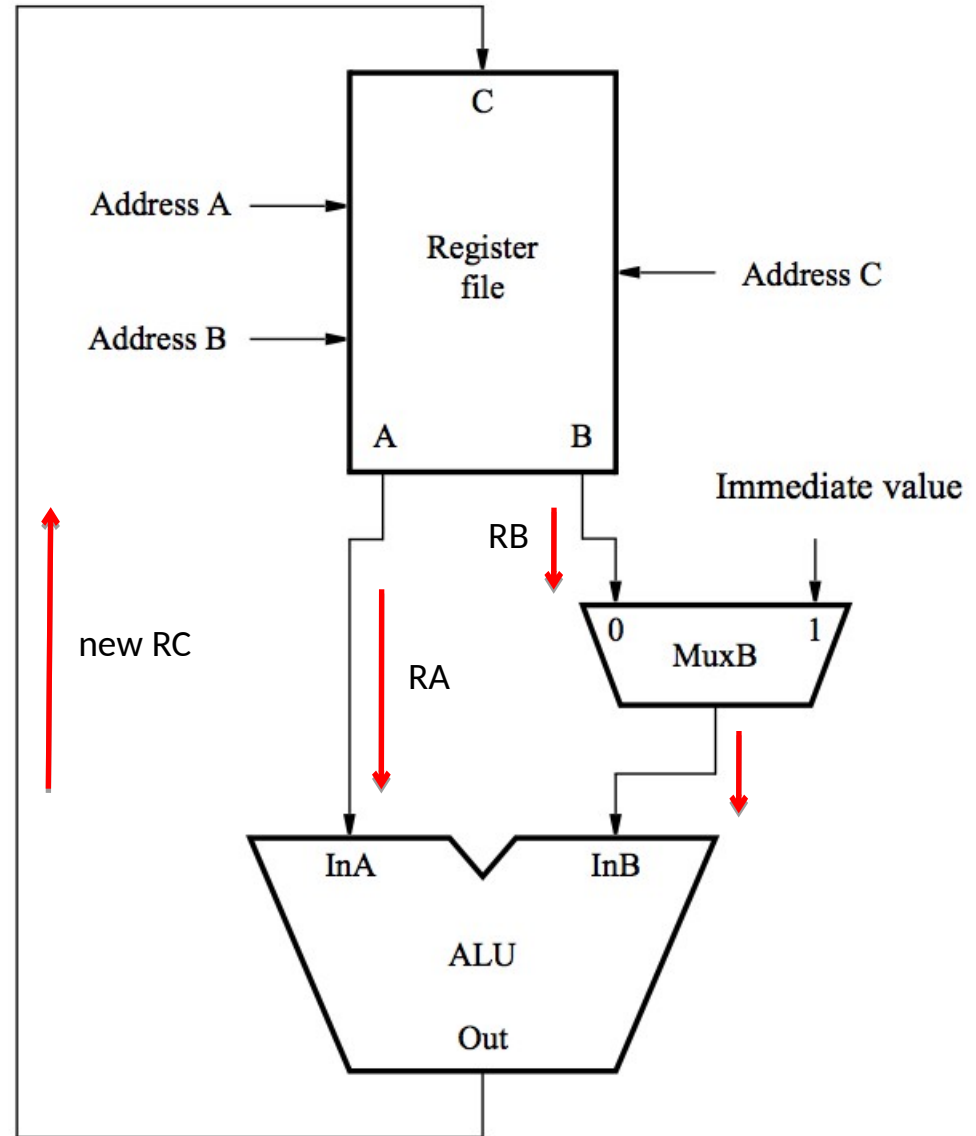- Both source operands and the destination location are in the register file.
- Conceptual single-cycle view of an arithmetic or logical instruction with two source operands in registers




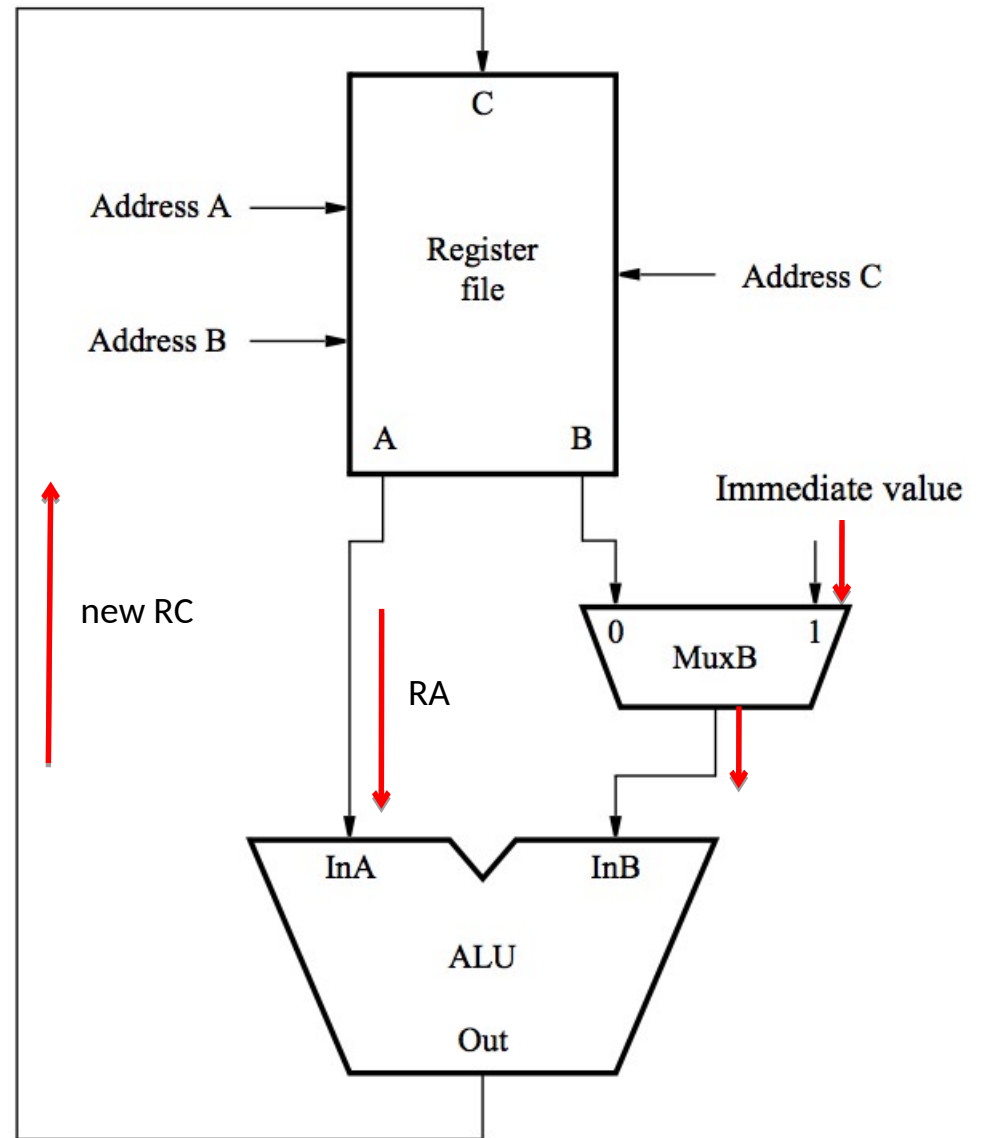- One of the source operands is the immediate value in IR




A 5-stage implementation of a RISC processor

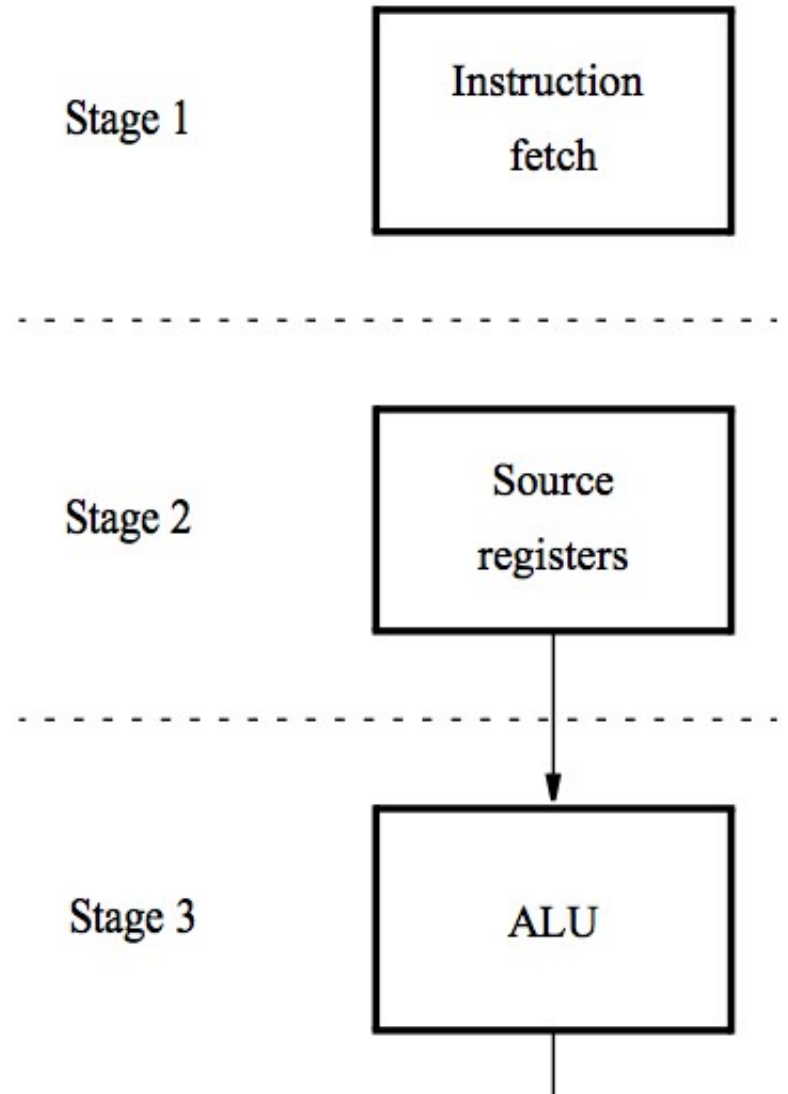- Instruction processing moves from stage to stage in every clock cycle, starting with fetch.
- The instruction is decoded and the source registers are read in stage 2.
- Computation takes place in the ALU in stage 3.




A 5-stage implementation of a RISC processor

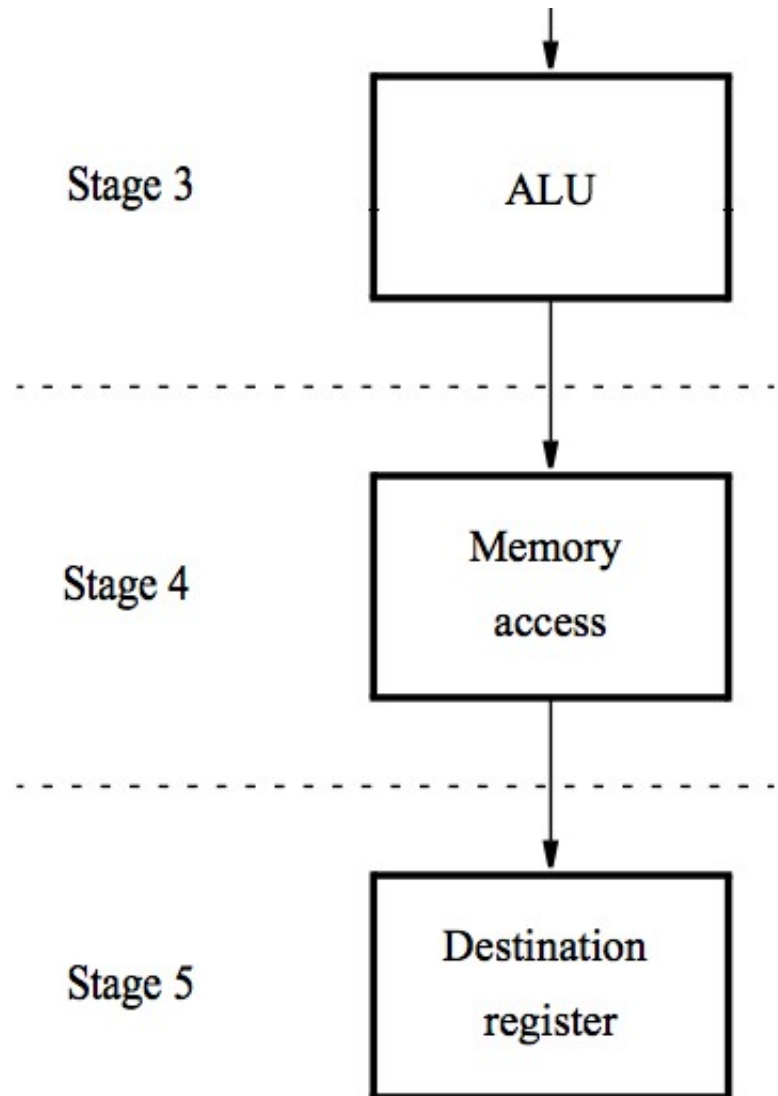- If a memory operation is involved, it takes place in stage 4.
- The result of the instruction is stored in the destination register in stage 5.




How can we decode the instruction and read the registers at the same time?

 
- In a RISC ISA, the register fields are always in the same positions in the instruction. If the registers were not needed by that instruction, the retrieved values will be ignored.



ADD R1, R3, R2

 

ADD R4, R5, #24

 


Load/Store encoding

Waiting for memory

- We have assumed that all memory accesses take one clock cycle. Is this realistic?
 - Mostly true if we use a cache!
- In the case of cache miss, the processor must be stalled to wait for the memory access to complete (a variable number of cycles)
- The processor-memory interface generates a signal called *Memory Function Completed (MFC)*
- *Processor extends the duration of the memory step (in units of clock cycles) until MFC is asserted*


The datapath – Stages 2 to 5

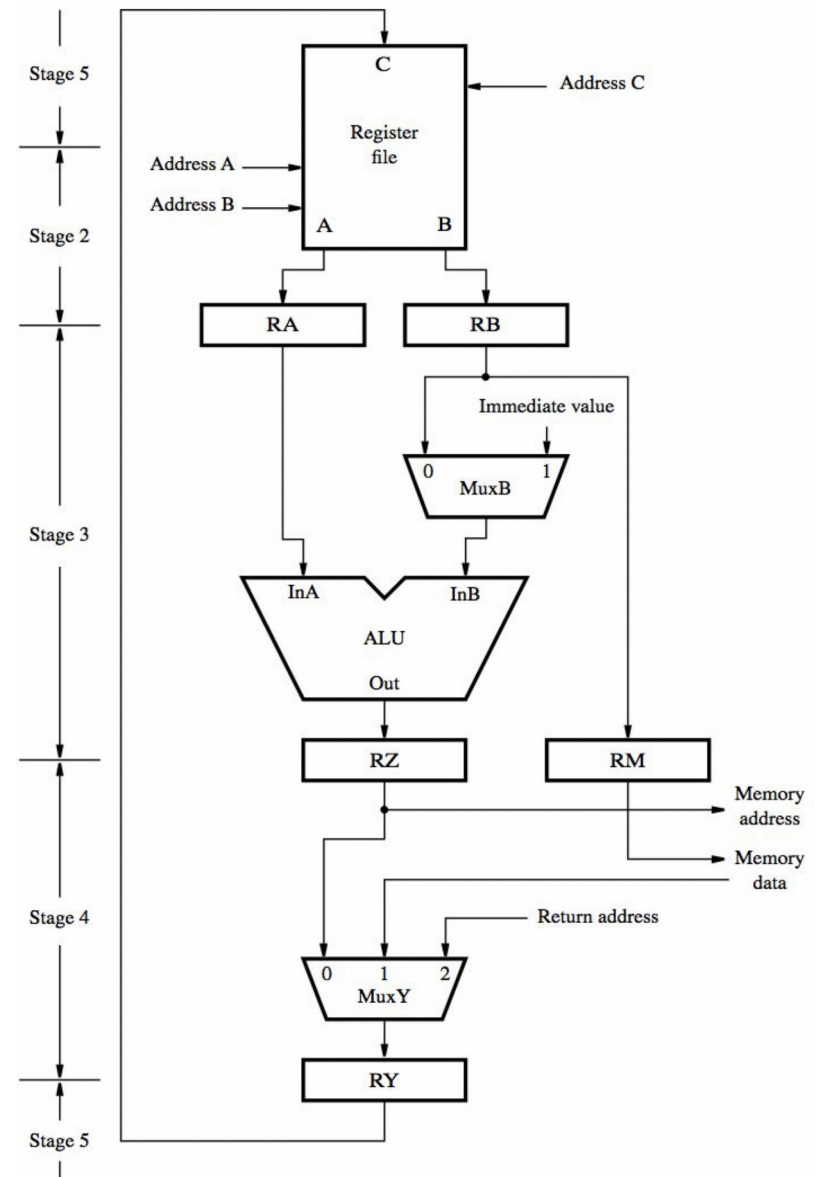- Register file, used in stages 2 and 5
- Multicycle: Inter-stage registers RA, RB, RZ, RY needed to carry data from one stage to the next
- ALU stage
- Memory stage
- Final stage to store result to the register file




Register file – Stages 2 & 5

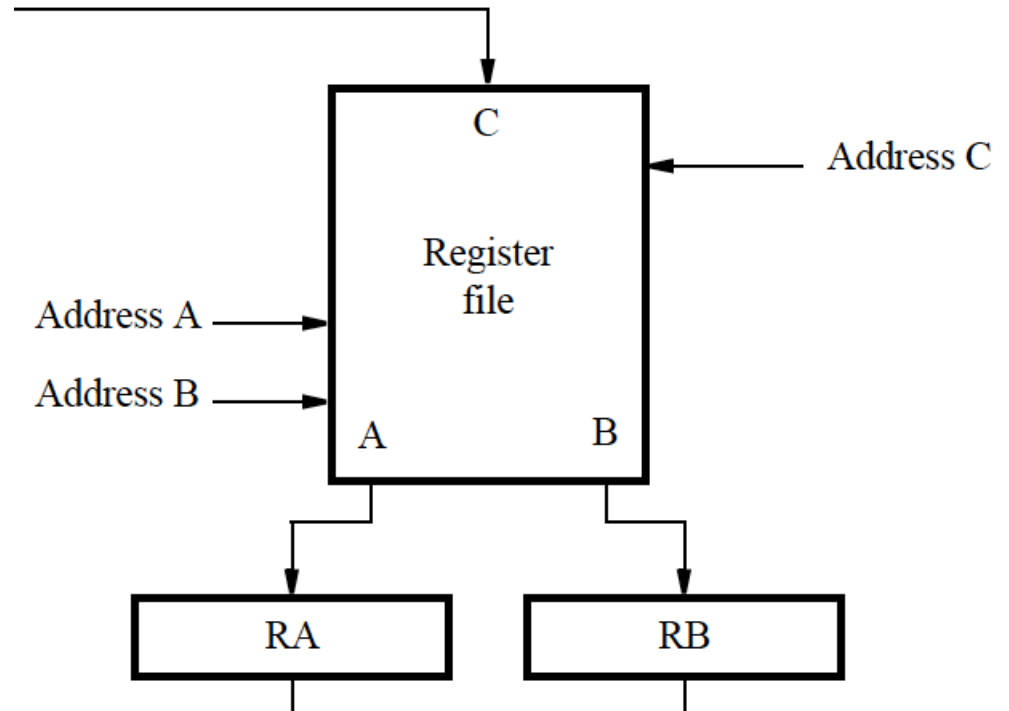- Address inputs are connected to the corresponding fields in IR
- Source registers are read in stage 2; their contents are stored in RA and RB
- In stage 5, the result of the instruction is stored in the destination register selected by Address C




ALU stage

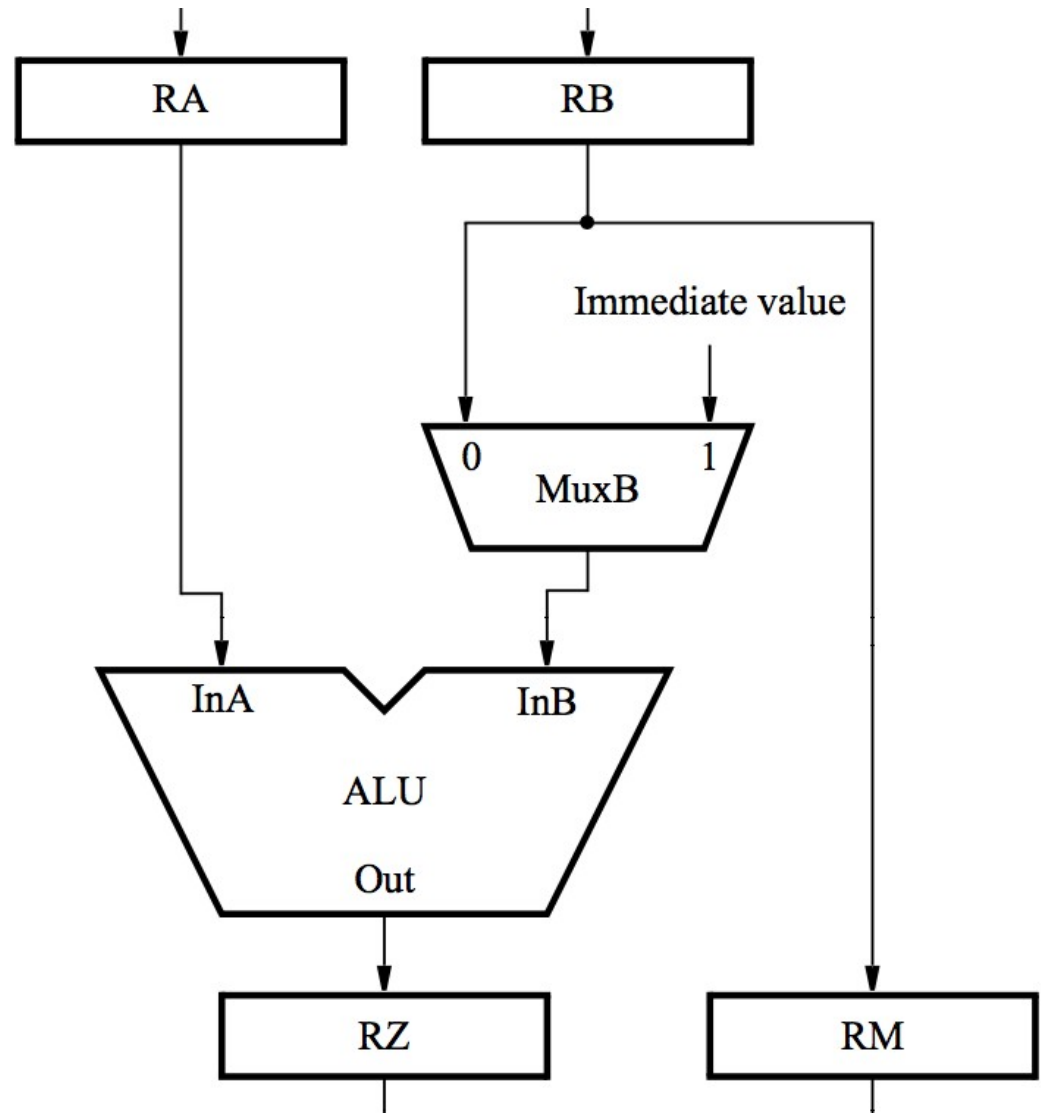- ALU performs calculation specified by the instruction.
- Multiplexer MuxB selects either RB or the Immediate field of IR
- Results stored in RZ
- Data to be written in the memory are transferred from RB to RM




Memory stage

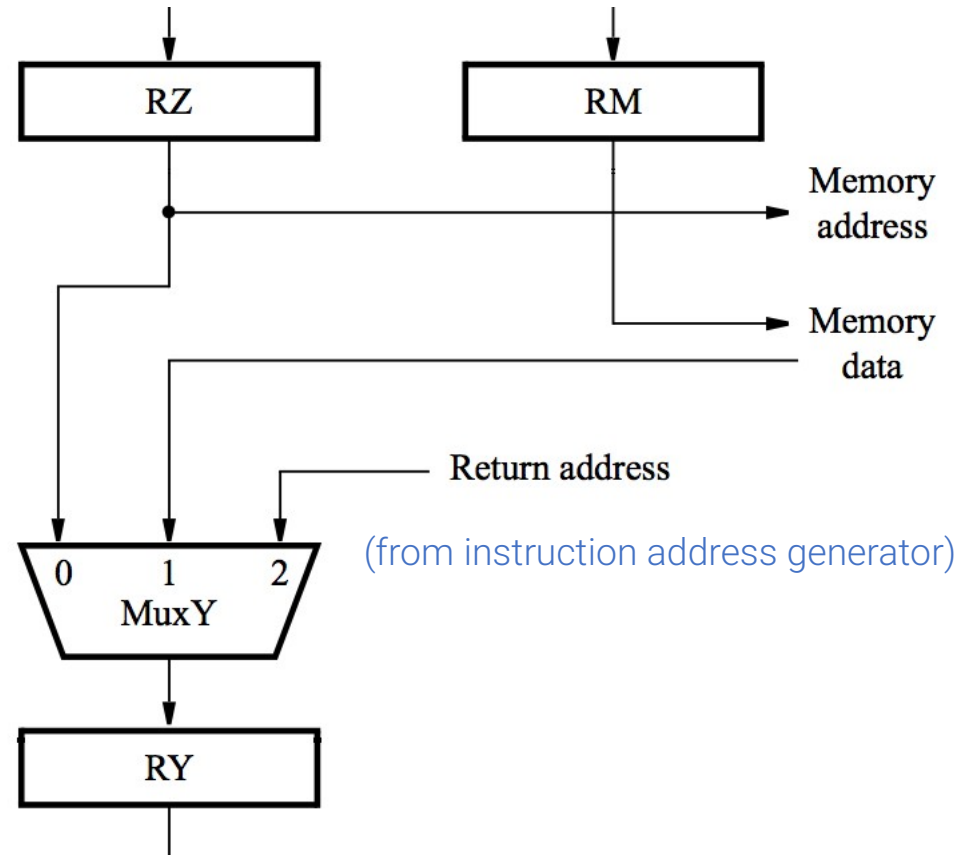- For a memory instruction, **RZ** provides memory address, and **MuxY** selects read data to be placed in **RY**.
- **RM** provides data for a memory write operation.
- For a calculation instruction, **MuxY** selects **RZ** to be placed in **RY**.
- Input 2 of **MuxY** is used in subroutine calls.



Memory address generation

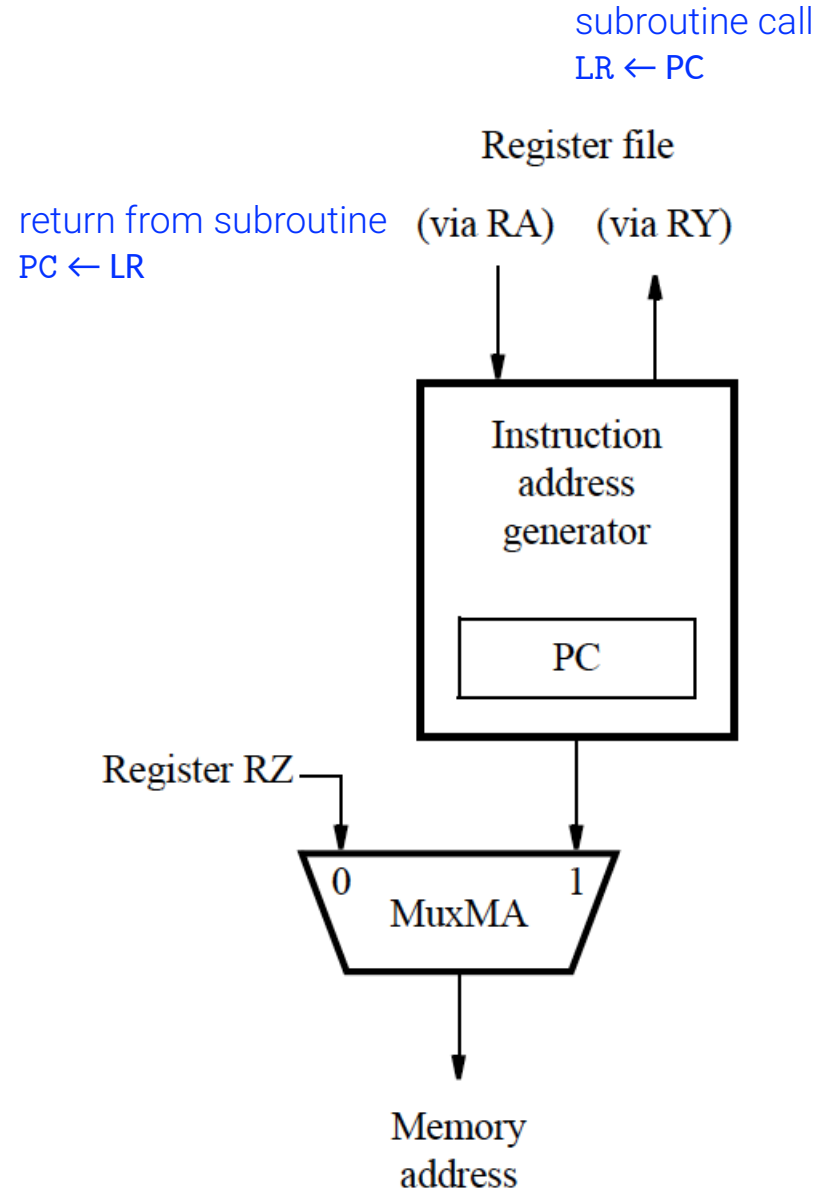- MuxMA selects the PC when fetching instructions.
- The Instruction address generator increments the PC after fetching an instruction.
- It also generates branch and subroutine addresses.
- MuxMA selects RZ when reading/writing data operands.




Processor control section

- When an instruction is read, it is placed in **IR**.
- The control circuitry decodes the instruction.
- It generates the control signals that drive all units.
- The Immediate block extends the immediate operand to 32 bits, according to the type of instruction


arithmetic: sign-extend

logic: zero padding

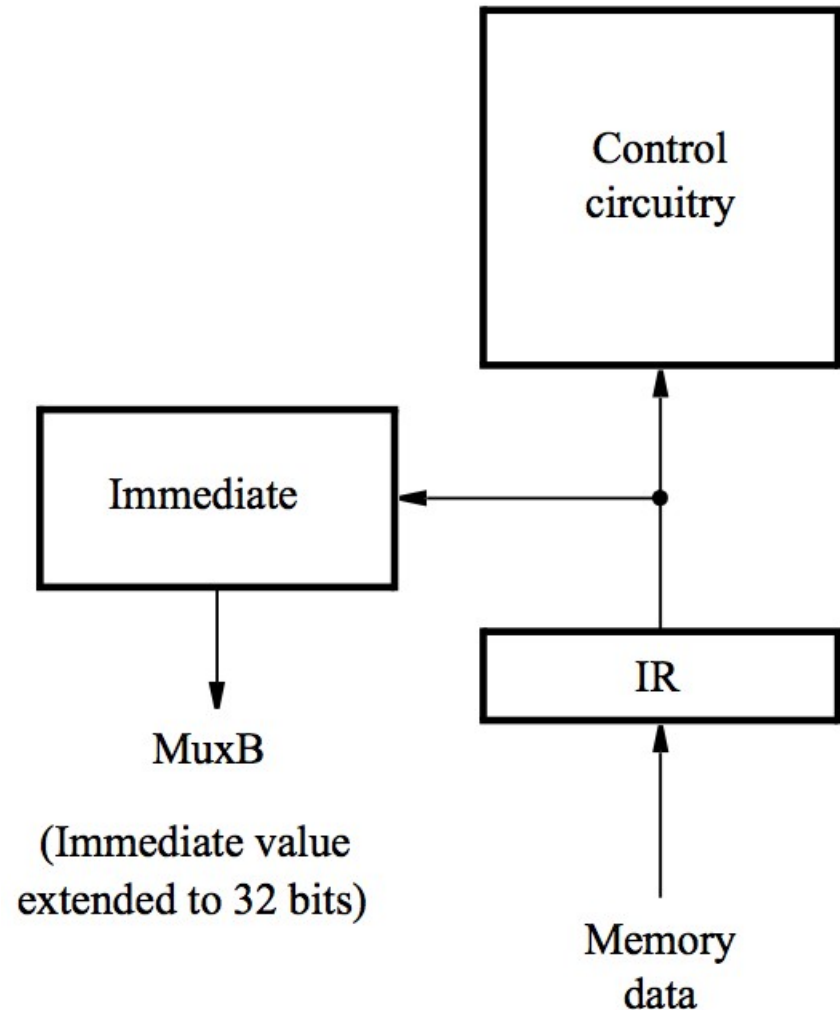


Instruction address generator

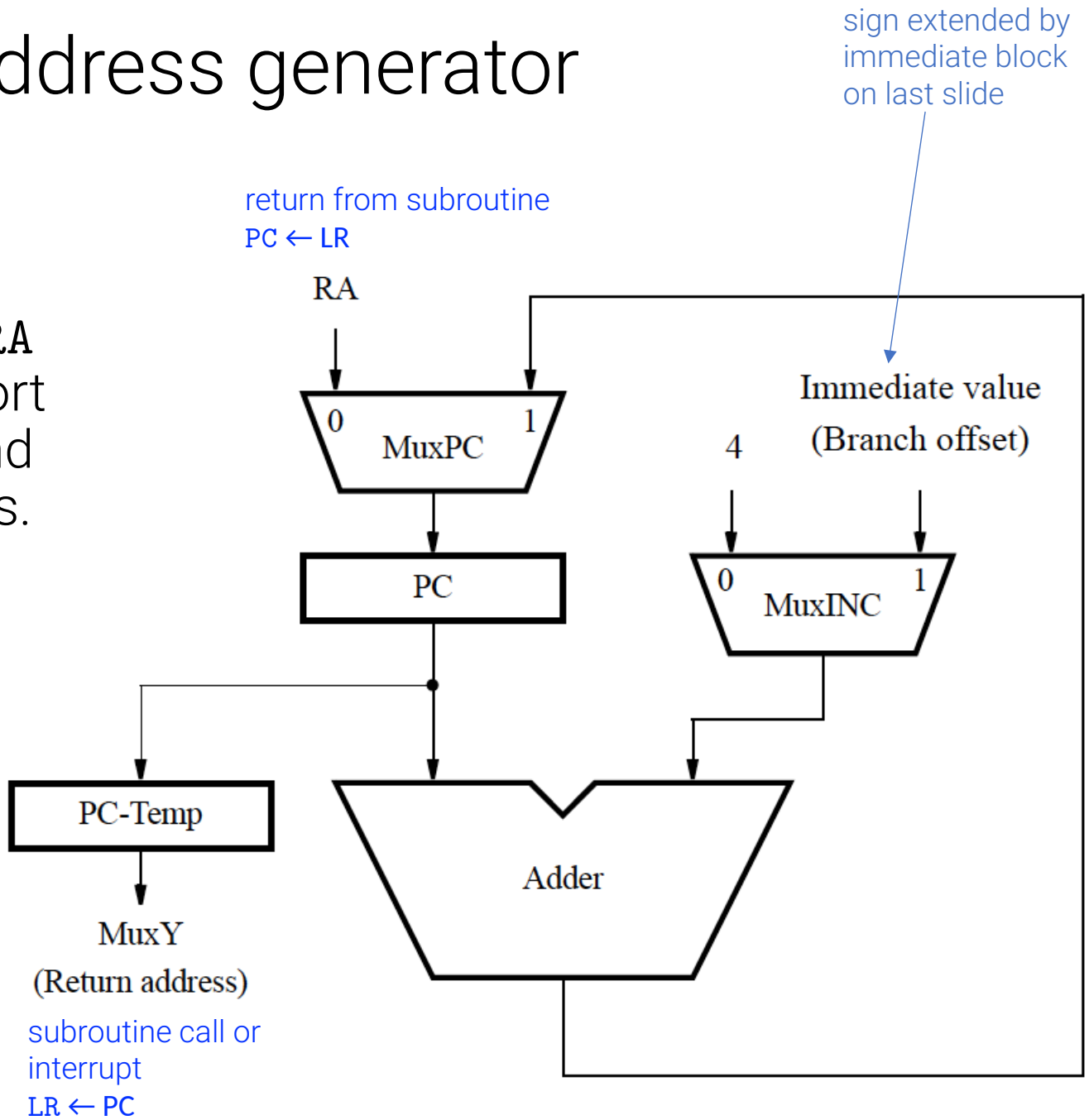- Connections to registers RY and RA are used to support subroutine call and return instructions.




Example: Add R3, R4, R5

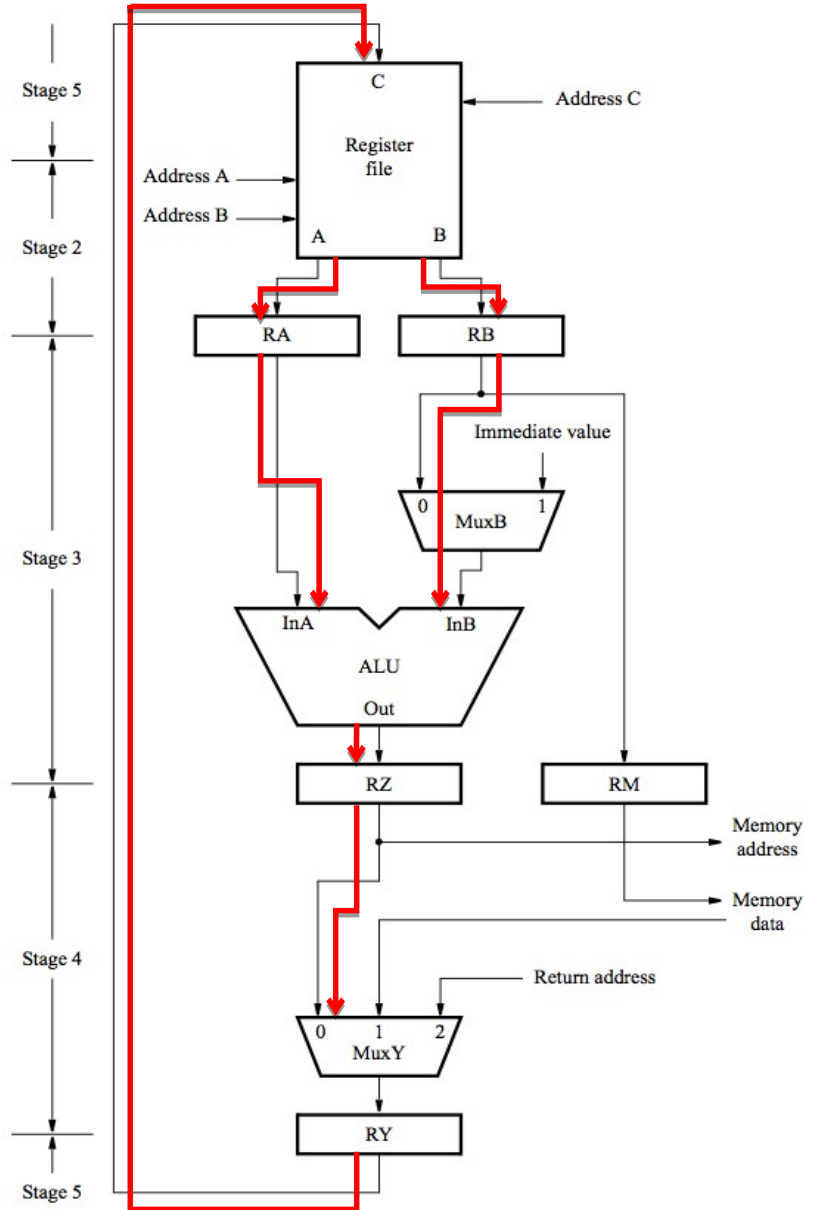1. Memory address \leftarrow PC,
 Read memory,
 IR \leftarrow Memory data, All of these actions happen in parallel
 PC \leftarrow PC + 4
2. Decode instruction,
 RA \leftarrow R4,
 RB \leftarrow R5
3. RZ \leftarrow RA + RB
4. RY \leftarrow RZ
5. R3 \leftarrow RY




Example: LDR R5, [R7, #X]

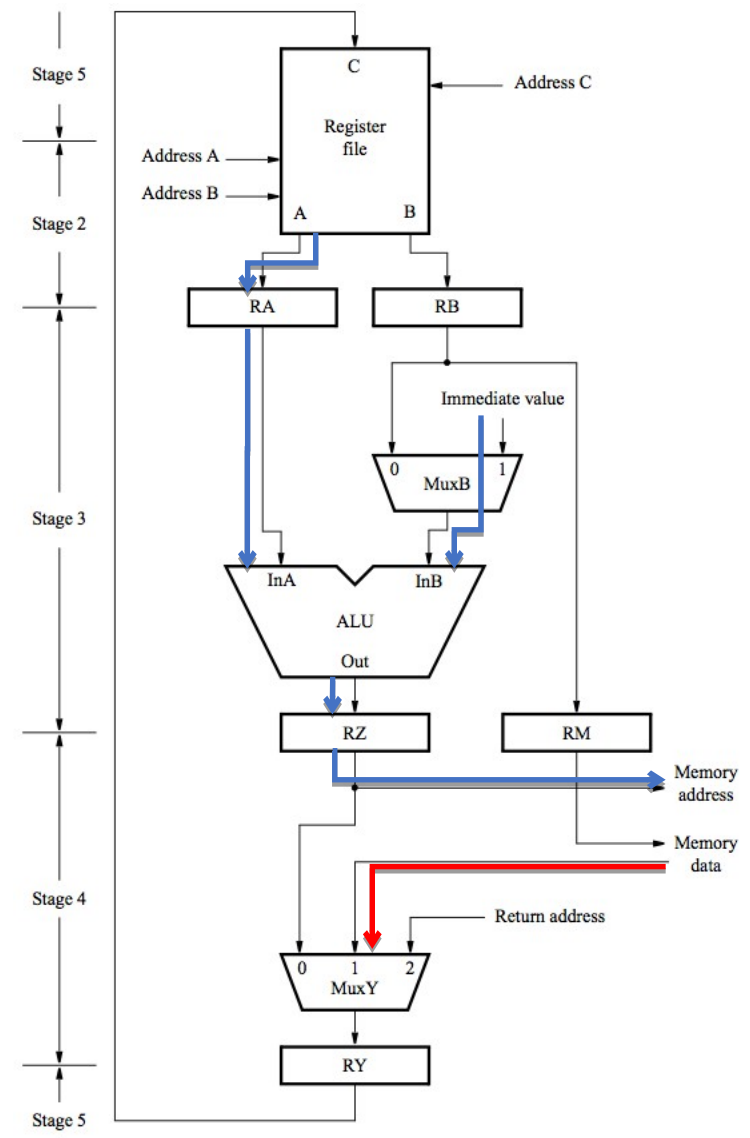- 1. Memory address \leftarrow PC, Read memory, IR \leftarrow Memory data, PC \leftarrow PC + 4
- 2. Decode instruction, RA \leftarrow R7
- 3. RZ \leftarrow RA + Immediate value X
- 4. Memory address \leftarrow RZ, Read memory, RY \leftarrow Memory data
- 5. R5 \leftarrow RY



Example: STR R6, [R8, #X]

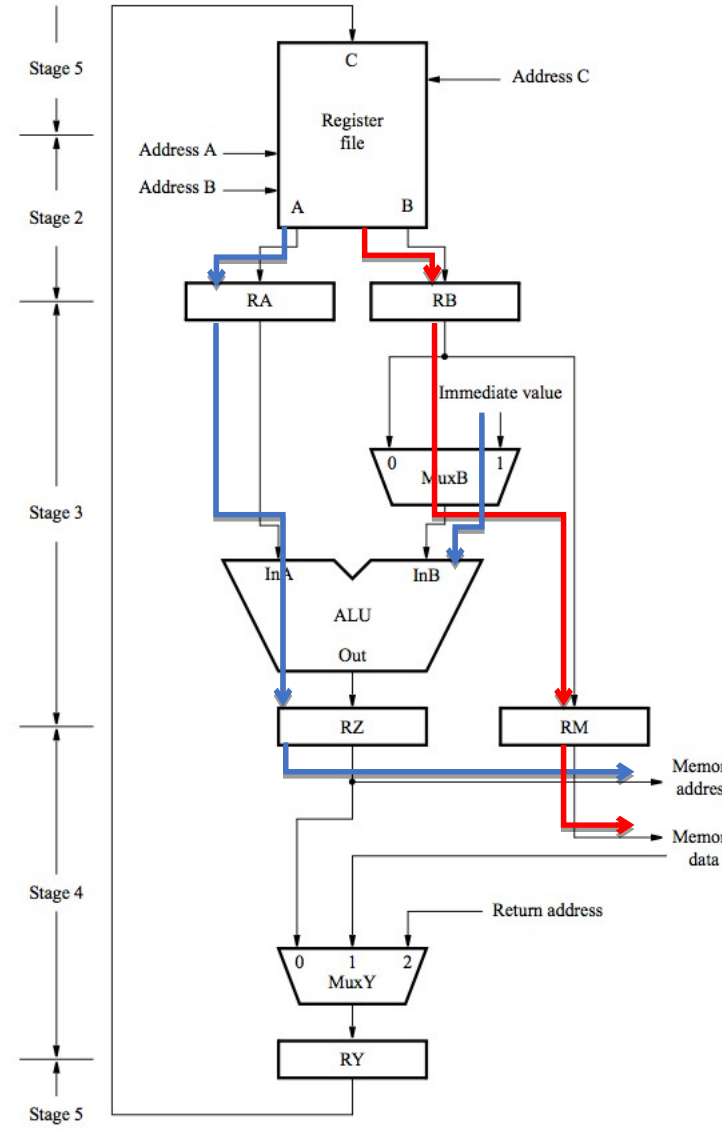1. Memory address \leftarrow PC,
Read memory,
IR \leftarrow Memory data,
PC \leftarrow PC + 4
2. Decode instruction,
RA \leftarrow R8,
RB \leftarrow R6
3. RZ \leftarrow RA + Immediate value X,
RM \leftarrow RB
4. Memory address \leftarrow RZ,
Memory data \leftarrow RM,
Write memory
5. No action



Unconditional branch

1. Memory address \leftarrow PC,
Read memory,
IR \leftarrow Memory data,
PC \leftarrow PC + 4
2. Decode instruction
3. PC \leftarrow PC + Branch offset
4. No action
5. No action

Conditional branch

- We will illustrate the generic RISC branch, that does not use condition codes.
- Instead, RISC branches compares values in registers and tests for some condition

e.g. `BEQ R5, R6, LOOP`


branches to LOOP if $[R5] = [R6]$

Conditional branch: BEQ R5, R6, LOOP

1. Memory address \leftarrow PC,
Read memory,
IR \leftarrow Memory data,
PC \leftarrow PC + 4
2. Decode instruction,
RA \leftarrow R5,
RB \leftarrow R6
3. RZ \leftarrow RA - RB,
If $ALU_{iszero} = 1$ then PC \leftarrow PC + Branch offset
4. No action
5. No action

ALU has flags for zero, positive, negative, overflow, carry out


ARM Datapath

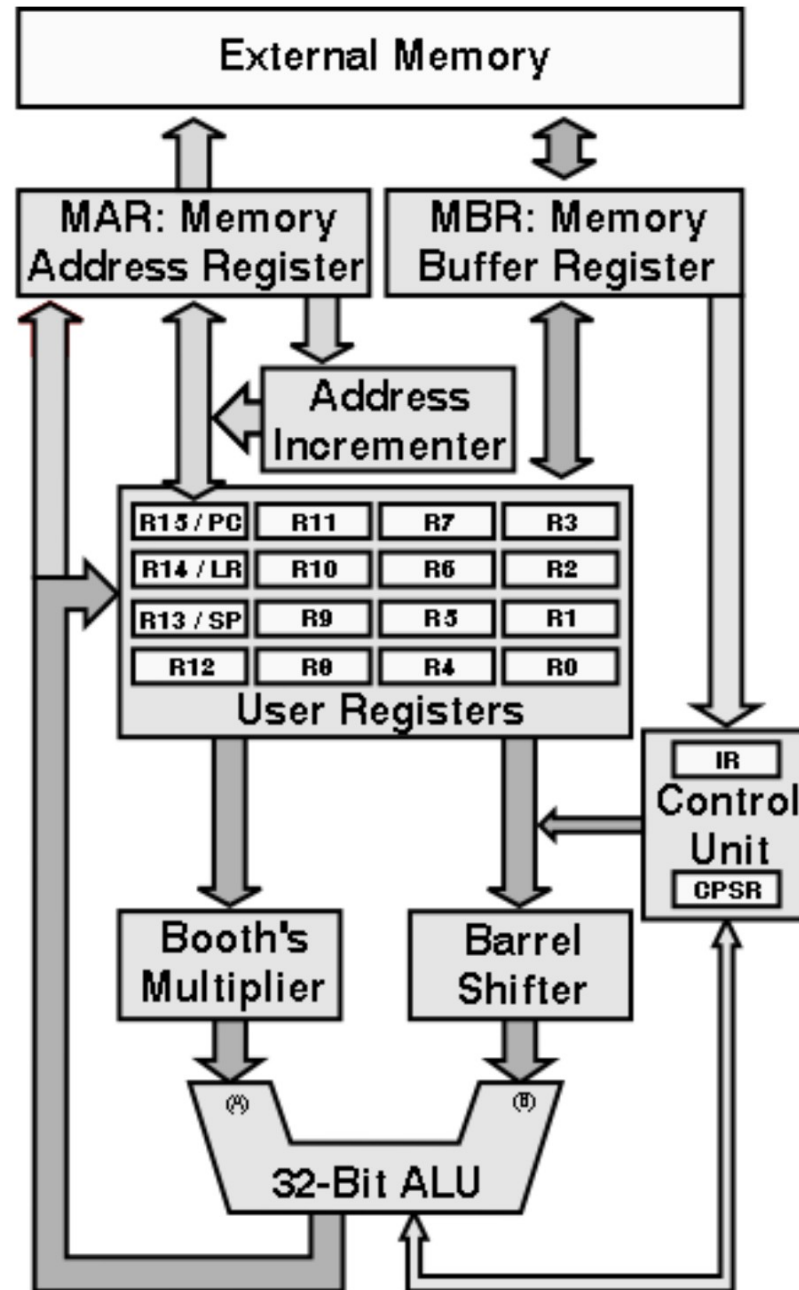


Control design

Textbook 5.5-5.7

Example RISC instruction format

 


(a) Register-operand format

 

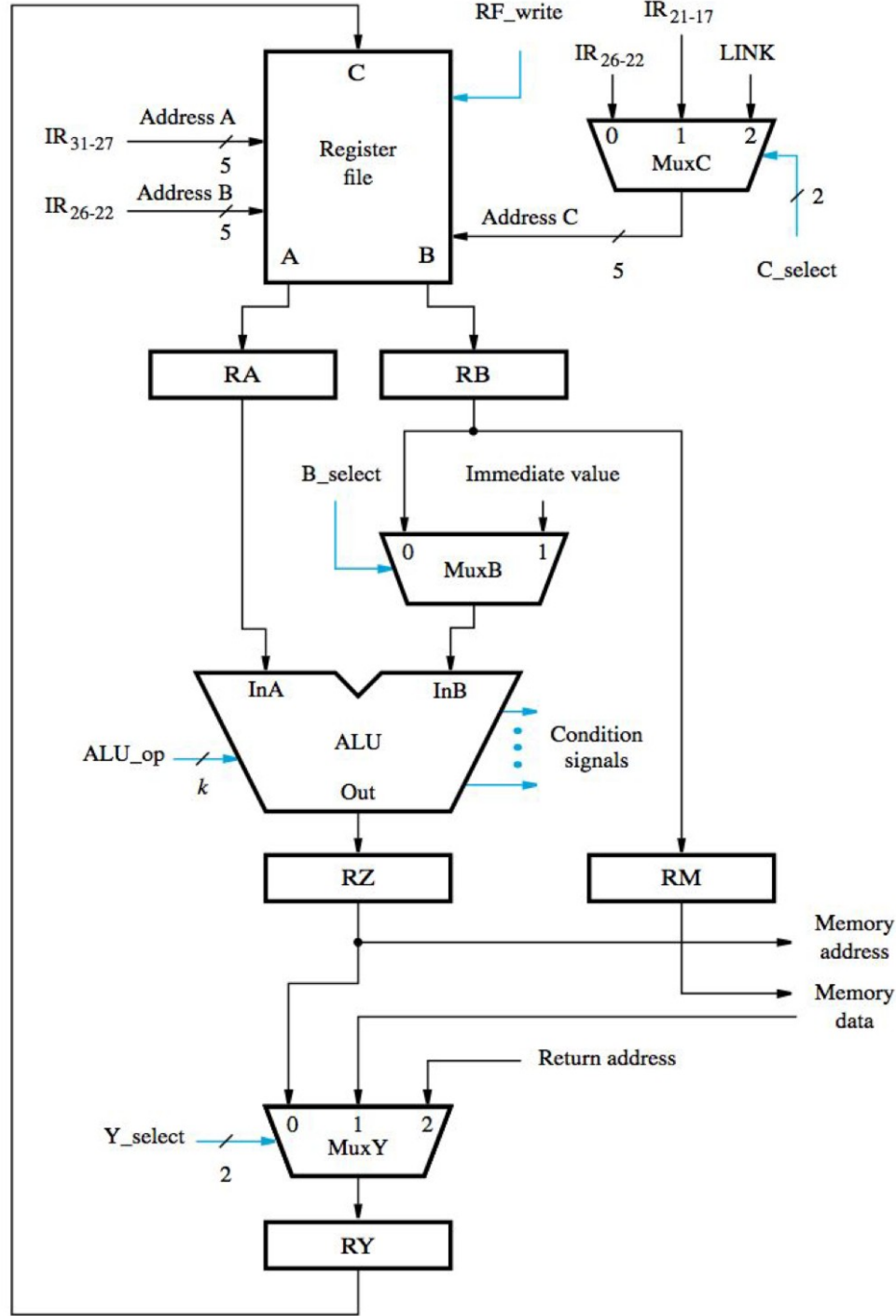
(b) Immediate-operand format

Control signals


- Select multiplexer inputs to guide the flow of data.
- Set the function performed by the ALU.
- Determine when data are written into the PC, the IR, the register file, and the memory.
- Inter-stage registers are always enabled because their contents are only relevant in the cycles for which the stages connected to the register outputs are active.



Memory and IR control signals

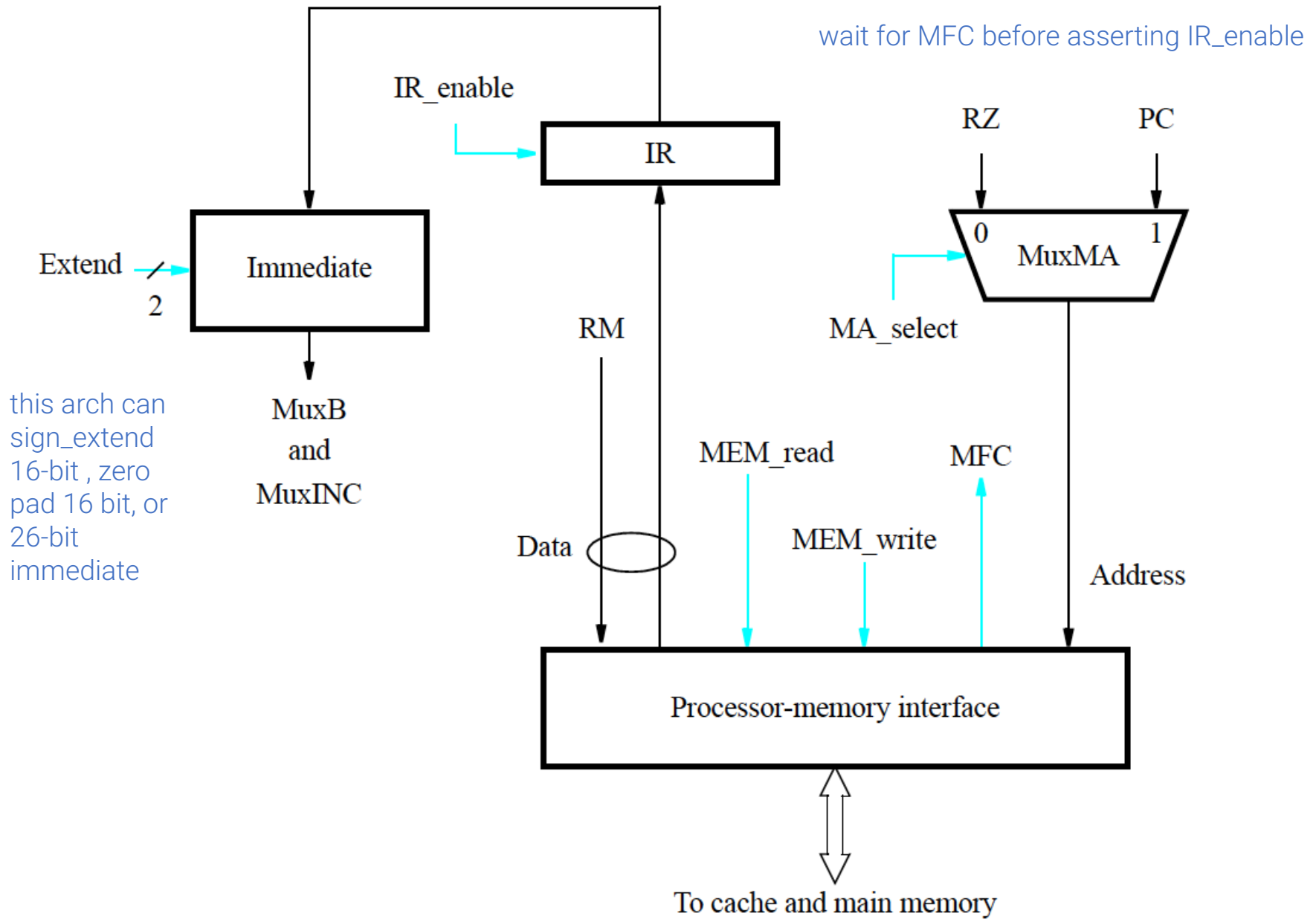

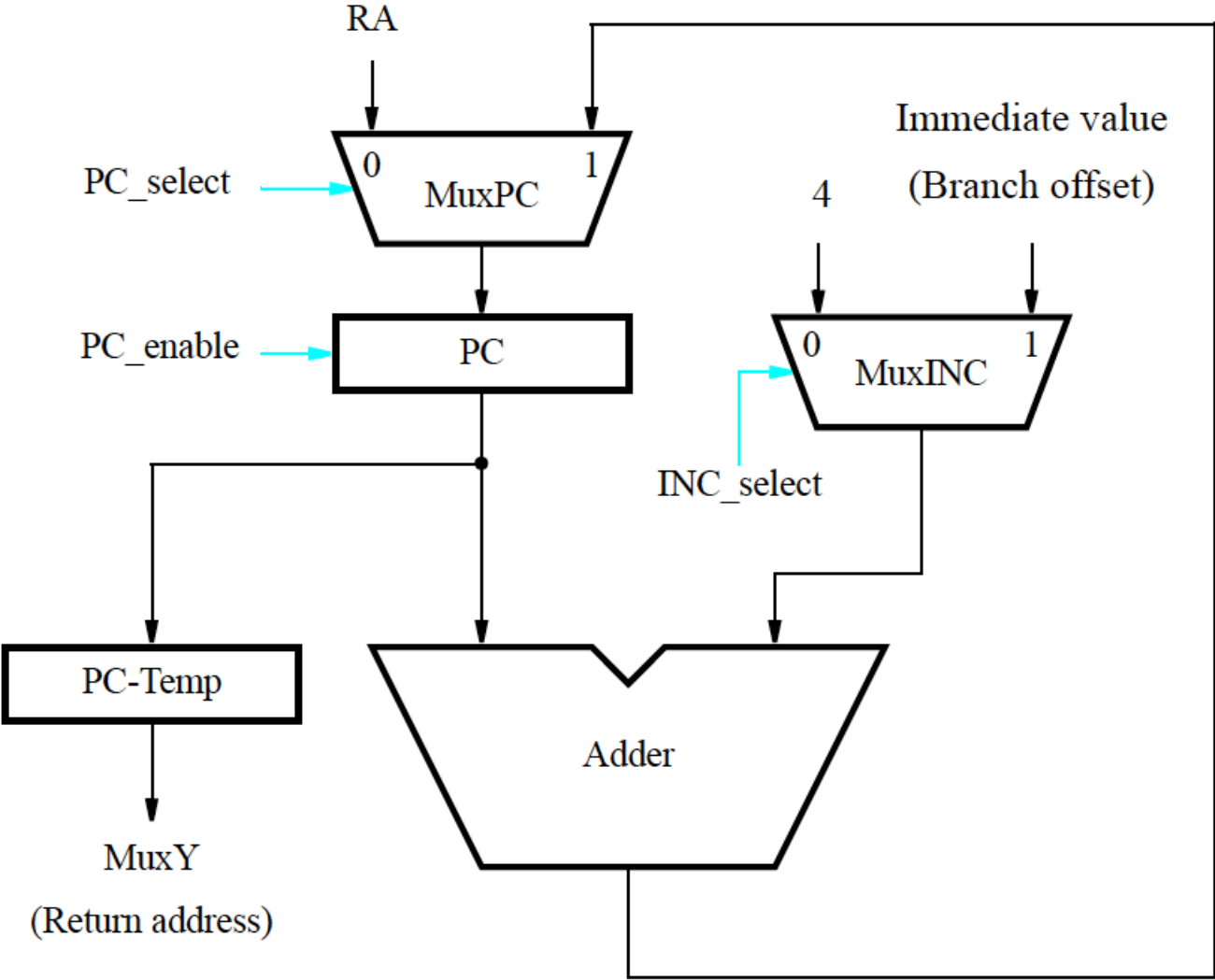Control signals of instruction address generator



Control signal generation

- The control unit generates the control signals so the actions in the datapath take place in the correct sequence and at the correct time.
- Two basic approaches:
 1. hardwired control
 2. microprogramming
- *Hardwired control* involves implementing a finite state machine (FSM).
- The state of the FSM is kept in a counter that keeps track of the execution step (one clock cycle / each of the 5 steps, unless a memory access takes more than one cycle)
- The inputs to the FSM are the IR, ALU result (result of a computation, comparison), and external inputs such as interrupt requests
- The outputs are the control signals

Hardwired generation of control signals

- Example: step 1 (fetch)

T1 = 1


MA_select = 1

MEM_read = 1

IR_enable = 1 when MFC asserted

PC incremented by 4 by setting INC_select to 0 and PC_select to 1

PC_enable = 1

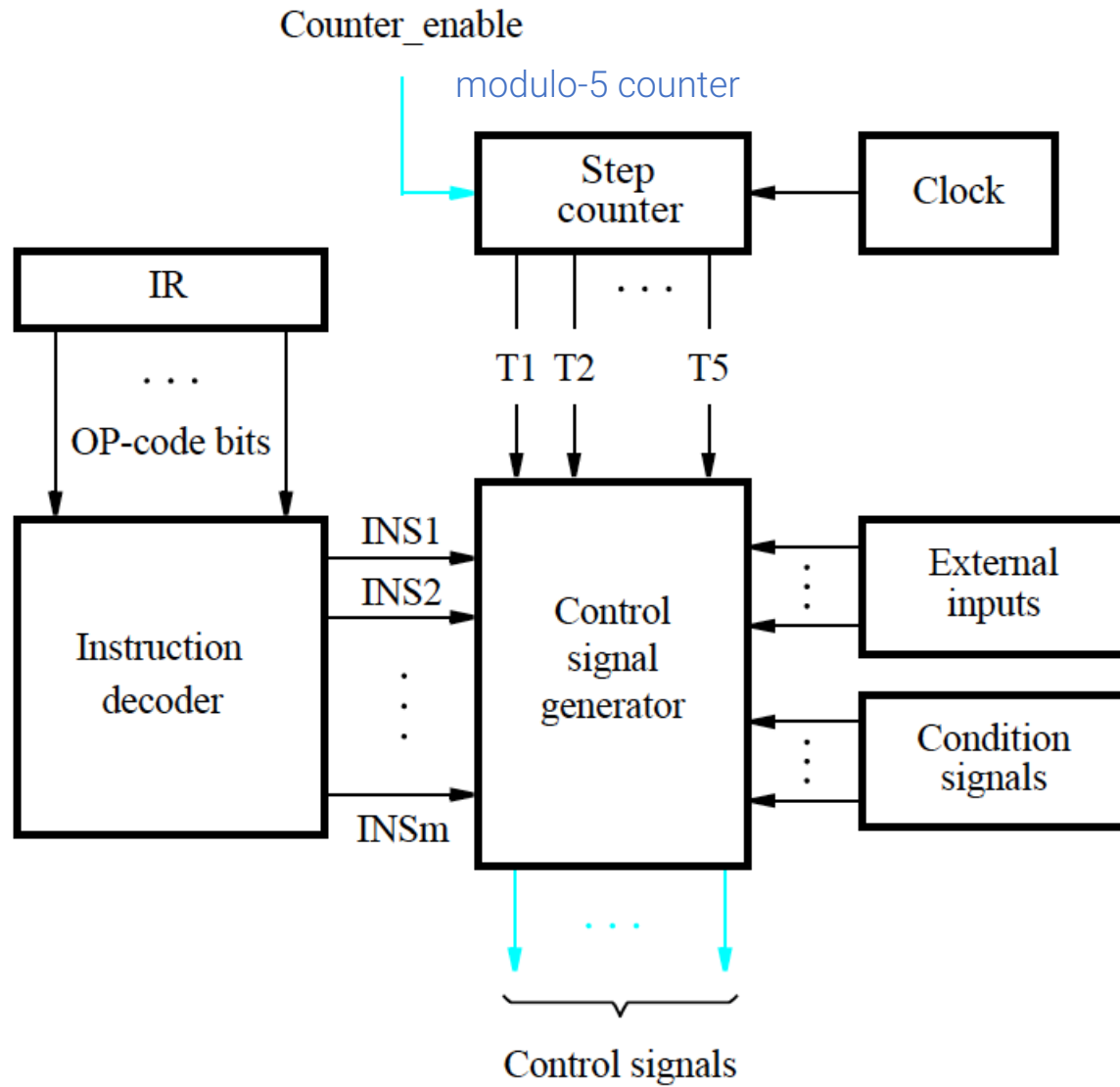

Example

- Wait until `MFC` to be asserted before incrementing step counter in a step in which `MEM_read` or `MEM_write` command is issued
- `Counter_enable` should be set to 1 in any step in which `WFMC` (wait for memory complete) is not asserted otherwise, it should be set to one when `MFC` is asserted
- What is the logic expression for the `Counter_enable` signal?

$$\text{Counter}_{\text{enable}} = \overline{\text{WFMC}} + \text{MFC}$$


Example

- Make sure the **PC** is incremented only once when a execution step is extended for more than one clock cycle
- **PC** should only be enabled when **MFC** is asserted, also in step 3 of branch instructions
- What is the logic expression for the **PC_enable** signal?

$$PC_{enable} = T1 \cdot MFC + T3 \cdot branch$$


CISC processors

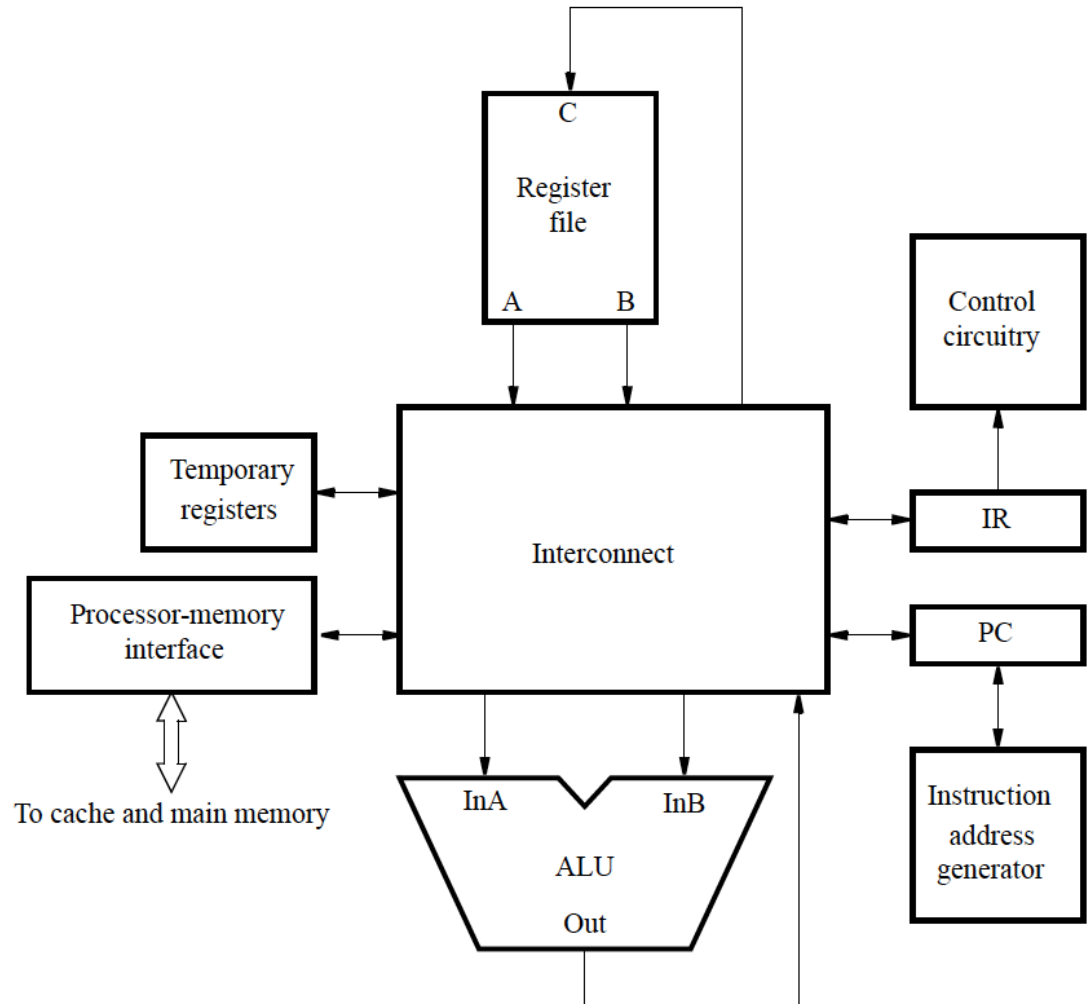- CISC-style processors have more complex instructions.
- Addressing modes that allow operands to be in memory, variable-length instructions




Bus

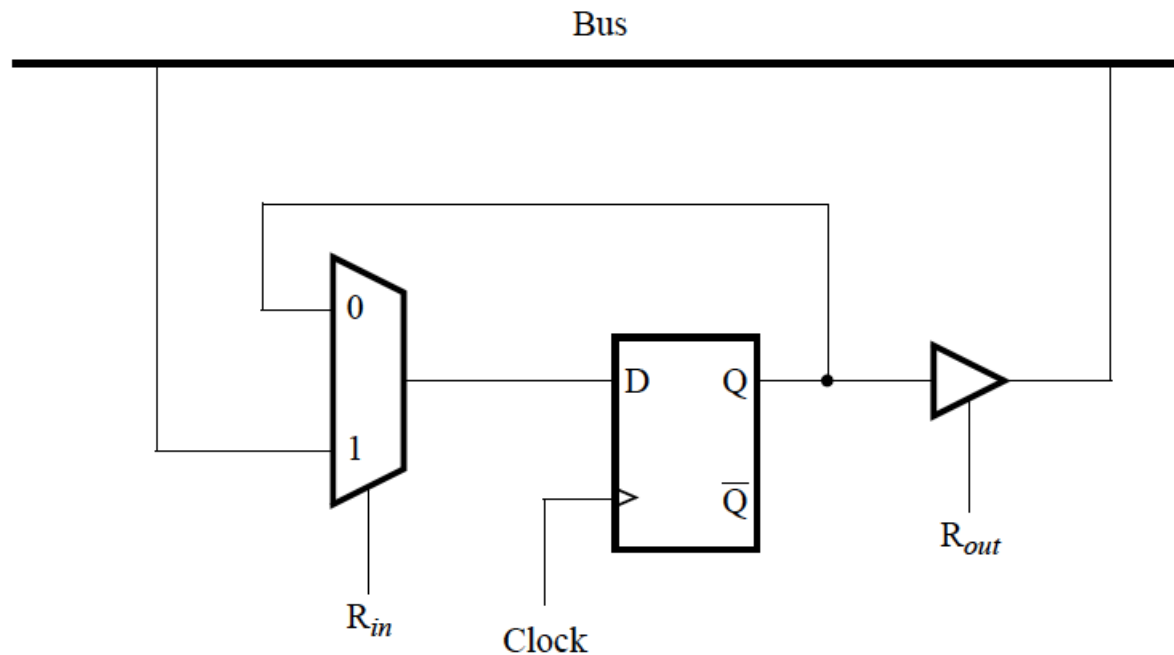- An example of an interconnection network.
- When functional units are connected to a common bus, tri-state drivers are needed.



A 3-bus CISC organization

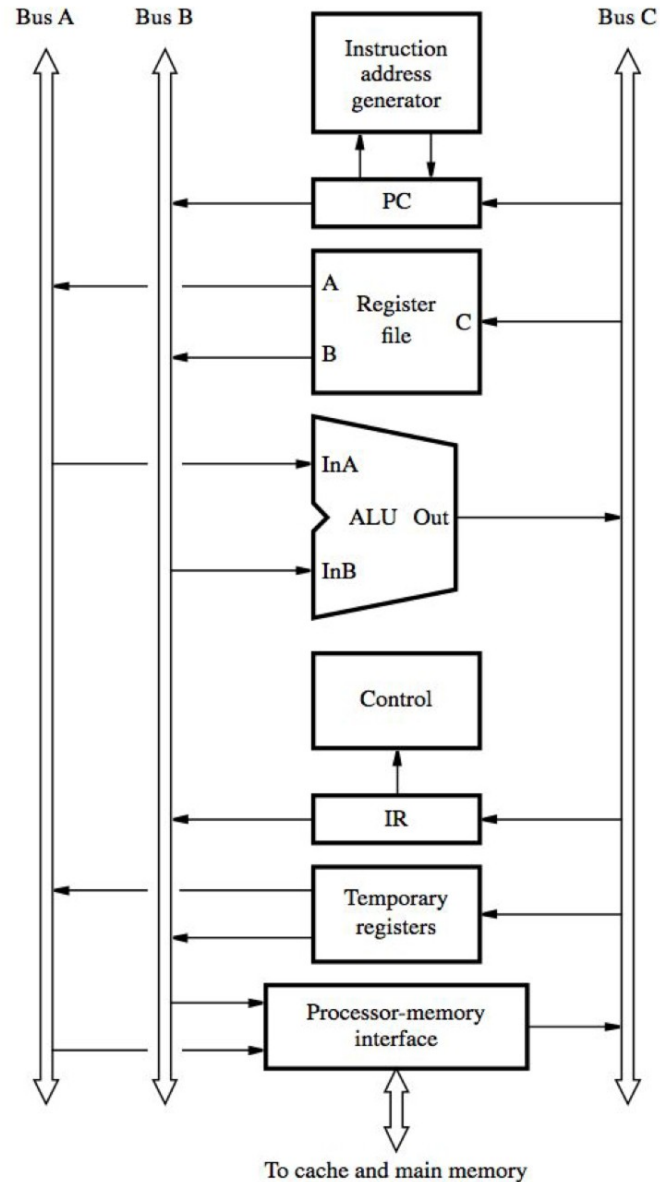addresses and
immediate
connections not
shown



Example: AND X(R7), R9 (2 word instruction)

fetch opcode

1. Memory address \leftarrow PC,
Read memory, Wait for MFC,
IR \leftarrow Memory data, PC \leftarrow PC + 4

2. Decode instruction

fetch second instruction word (X)


3. Memory address \leftarrow PC,
Read memory, Wait for MFC,
Temp1 \leftarrow Memory data, PC \leftarrow PC + 4

4. Temp2 \leftarrow Temp1 + R7

5. Memory address \leftarrow Temp2,
Read memory, Wait for MFC,
Temp1 \leftarrow Memory data


6. Temp1 \leftarrow Temp1 AND R9

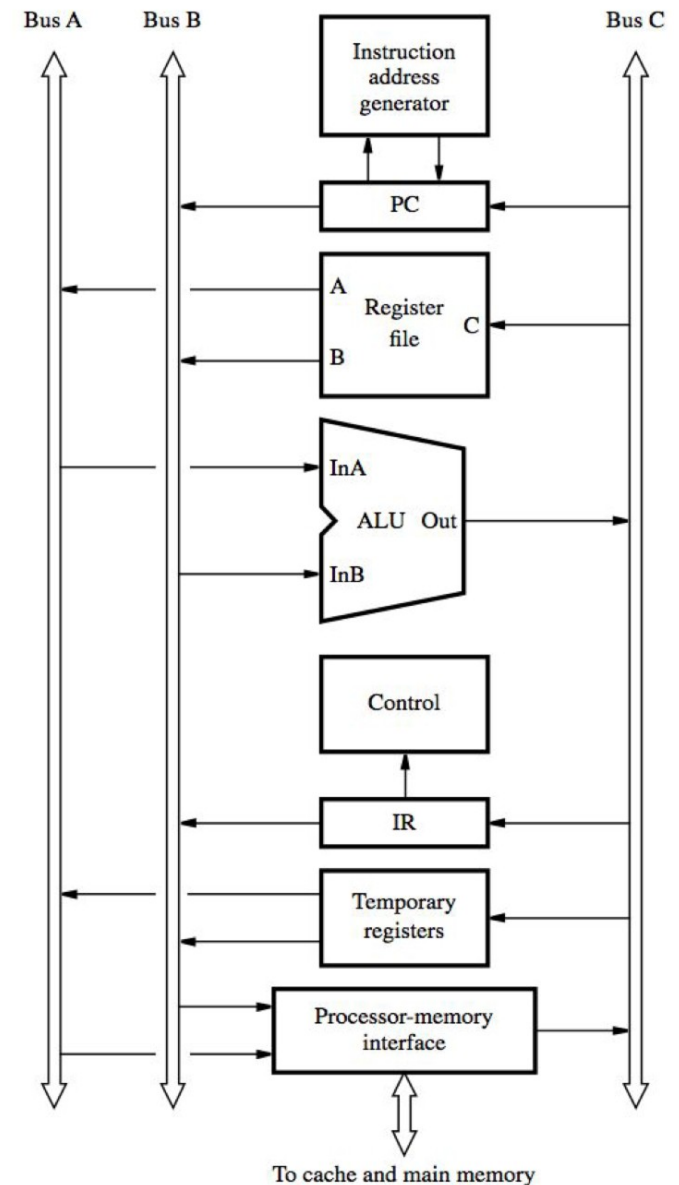7. Memory address \leftarrow Temp2,
Memory data \leftarrow Temp1,
Write memory, Wait for MFC



Microprogrammed control

- *Microprogramming* is a software-based approach for the generation of control signals.
- The values of the control signals for each clock period are stored in a *microinstruction* (control word) in a special memory.
- A processor instruction is implemented by a sequence of microinstructions.
- From decoding of an instruction in **IR**, the control circuitry executes the corresponding sequence of microinstructions.
- μ PC maintains the location of the current microinstruction.

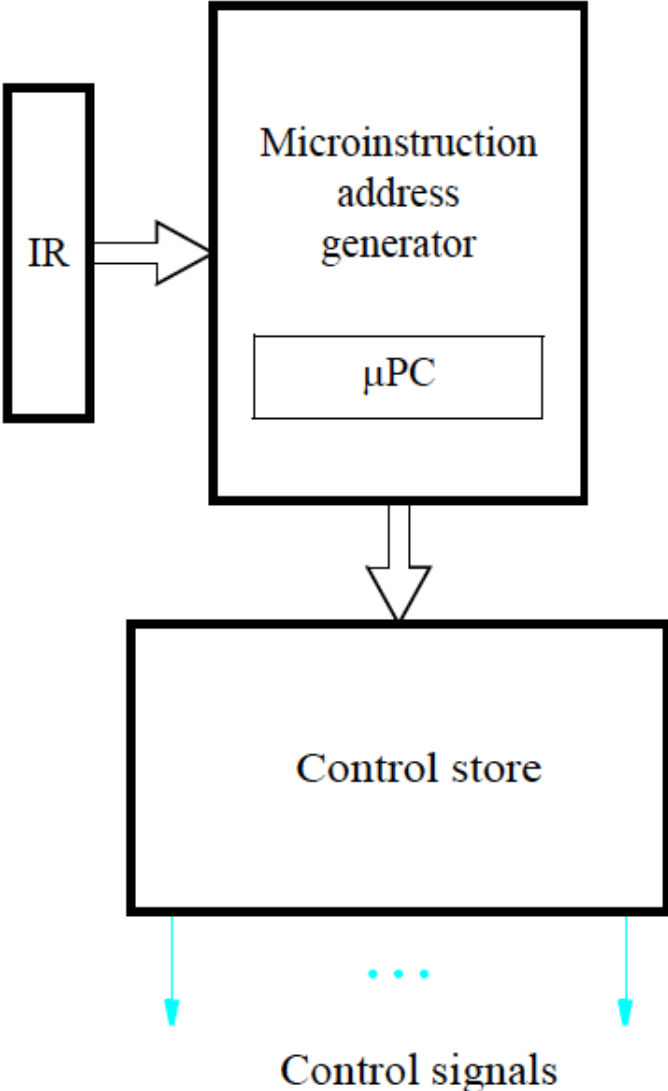

Microprogramming

- Microprogramming provides the flexibility needed to implement more complex instructions in CISC processors.
- However, reading and executing microinstructions incurs undesirably long delays in high-performance processors.

Pipelining

Textbook 6.1-6.7

Example

3 hours to complete one load

Wash

Dry


Fold

Example

6 hours to complete two loads




Example

 

 Example


3 hours to complete one load
1 load completes every hour
6 hours to complete 4 loads



What is pipelining?


- Pipelining is applying the "assembly line" concept to the execution of instructions
- Multiple instructions can be executed simultaneously !
- Divide the instruction into distinct steps (e.g. 5 steps)
- Overlap the execution of the five steps by allowing the hardware for each step to work on the next instruction in the program after it is finished working on the current instruction

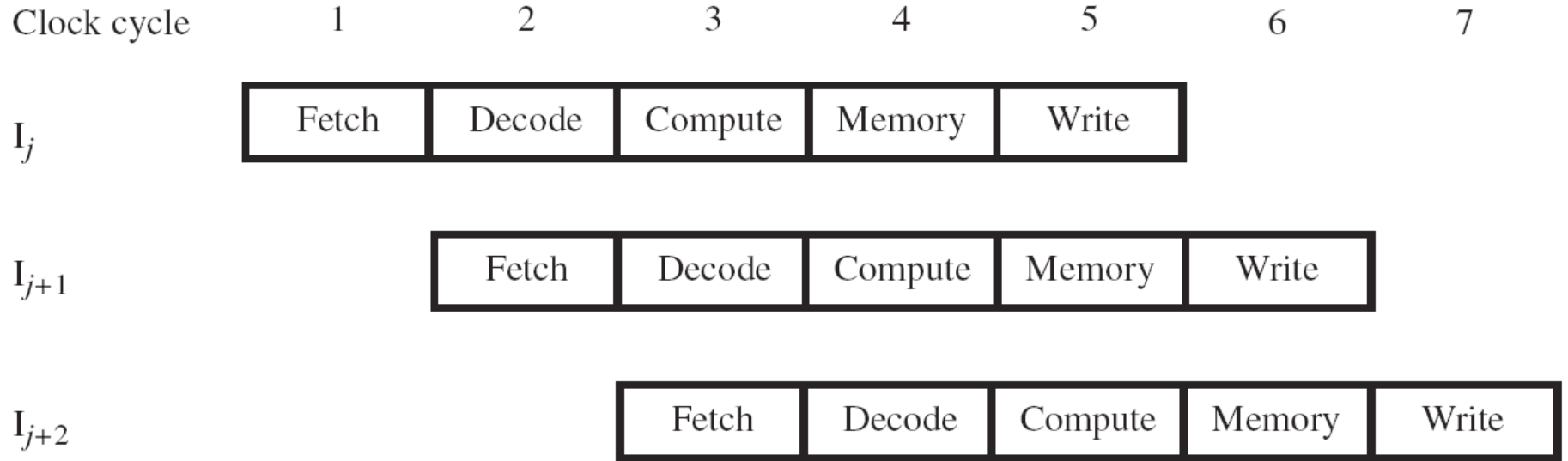Each instruction still takes 5 cycles to execute, but the rate is 1 instruction per cycle



Pipeline Organization

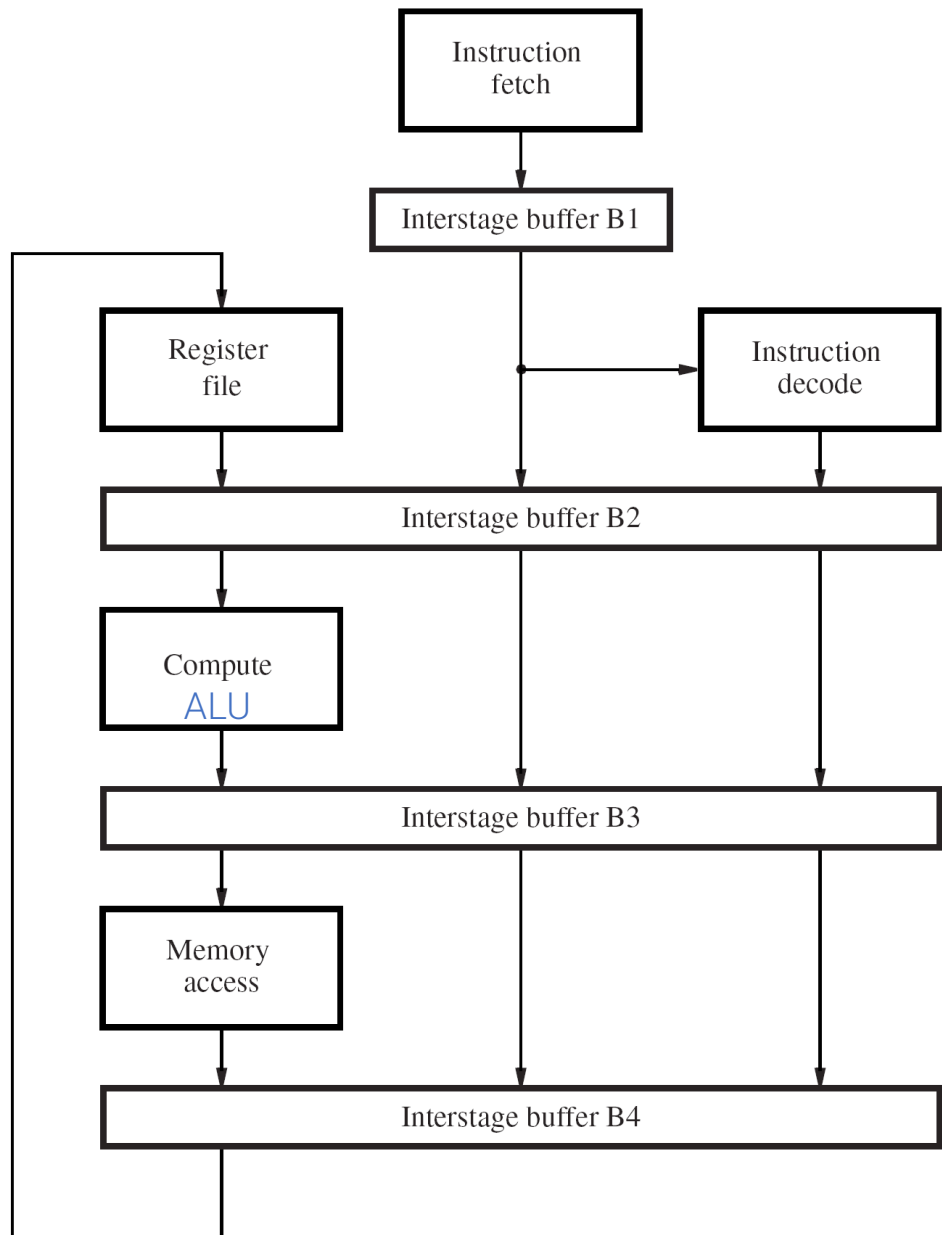- Use program counter (PC) to fetch instructions
- A new instruction enters pipeline every cycle
- Carry along instruction-specific information as instructions flow through the different stages
- Use *interstage buffers* or *pipeline registers* to hold this information
- These buffers incorporate RA, RB, RM, RY, RZ, IR, and PC-Temp registers
- The buffers also hold control signal settings



Datapath operands
and results

Source/destination
register identifiers
and other information


Control signals
for different stages

Data Dependencies

ADD	R2, R3, R7
SUB	R9, R2, R8

- Destination R2 of Add is a source for Subtract
- There is a **data dependency** between them because R2 carries data from Add to Subtract
- On *non*-pipelined datapath, result is available in R2 because Add completes before Subtract

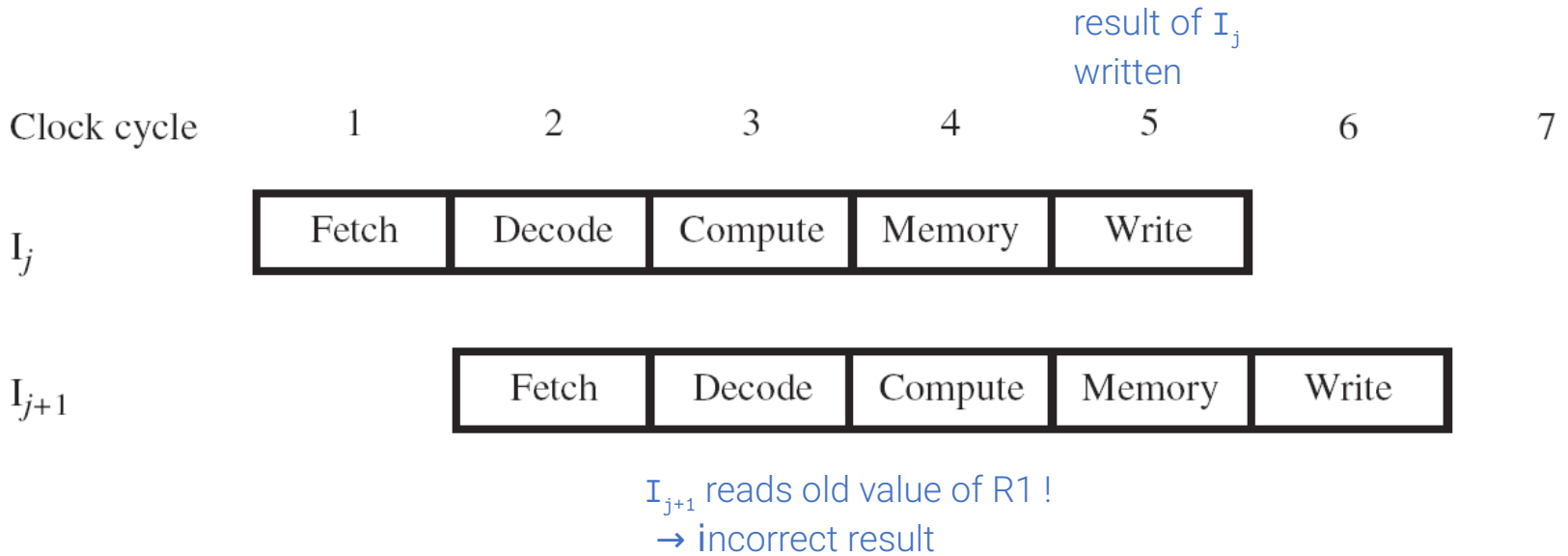
I_j : ADD R2, R3, R7
 I_{j+1} : SUB R9, R2, R8



- The pipeline does not allow the simultaneous execution of these particular instructions because of the data dependency
- This is called a *data hazard*


Stalling the Pipeline

 - With pipelined execution, old value is still in register R2 when Subtract is in Decode stage
- So *stall* Subtract for 3 cycles in Decode stage
- New value of R2 is then available in cycle 6




Details for Stalling the Pipeline

 - Control circuitry must recognize dependency while Subtract is being decoded in cycle 3
- Interstage buffers carry register identifiers for source(s) and destination of instructions
- In cycle 3, compare destination identifier in Compute stage against source(s) in Decode
- R2 matches, so Subtract kept in Decode while Add allowed to continue normally



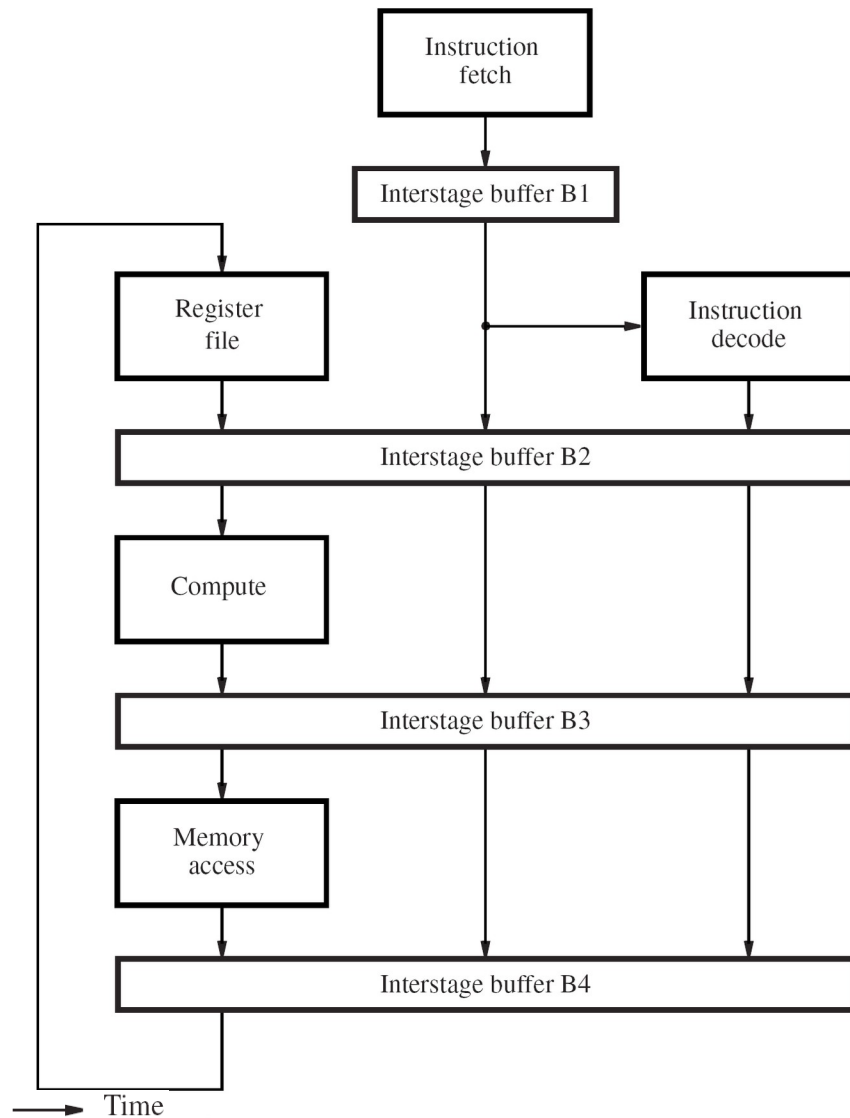- Stall the Subtract instruction for 3 cycles by holding interstage buffer B1 contents steady
- But what happens after Add leaves Compute?
- Control signals are set in cycles 3 to 5 to create an *implicit* **NOP** (No-operation) in Compute
- NOP control signals in interstage buffer B2 create a cycle of idle time in each later stage
- The idle time from each NOP is called a *bubble*



Clock cycle

1 2 3 4 5 6 7 8 9

ADD R2, R3, R7




SUB R9, R2, R8





Can we avoid stalls?

 
- *Operand forwarding* handles some dependencies without the penalty of stalling the pipeline
- For the preceding sequence of instructions, new value for R2 is available at end of cycle 3
- *Forward* value to where it is needed in cycle 4




Forwarding hardware

 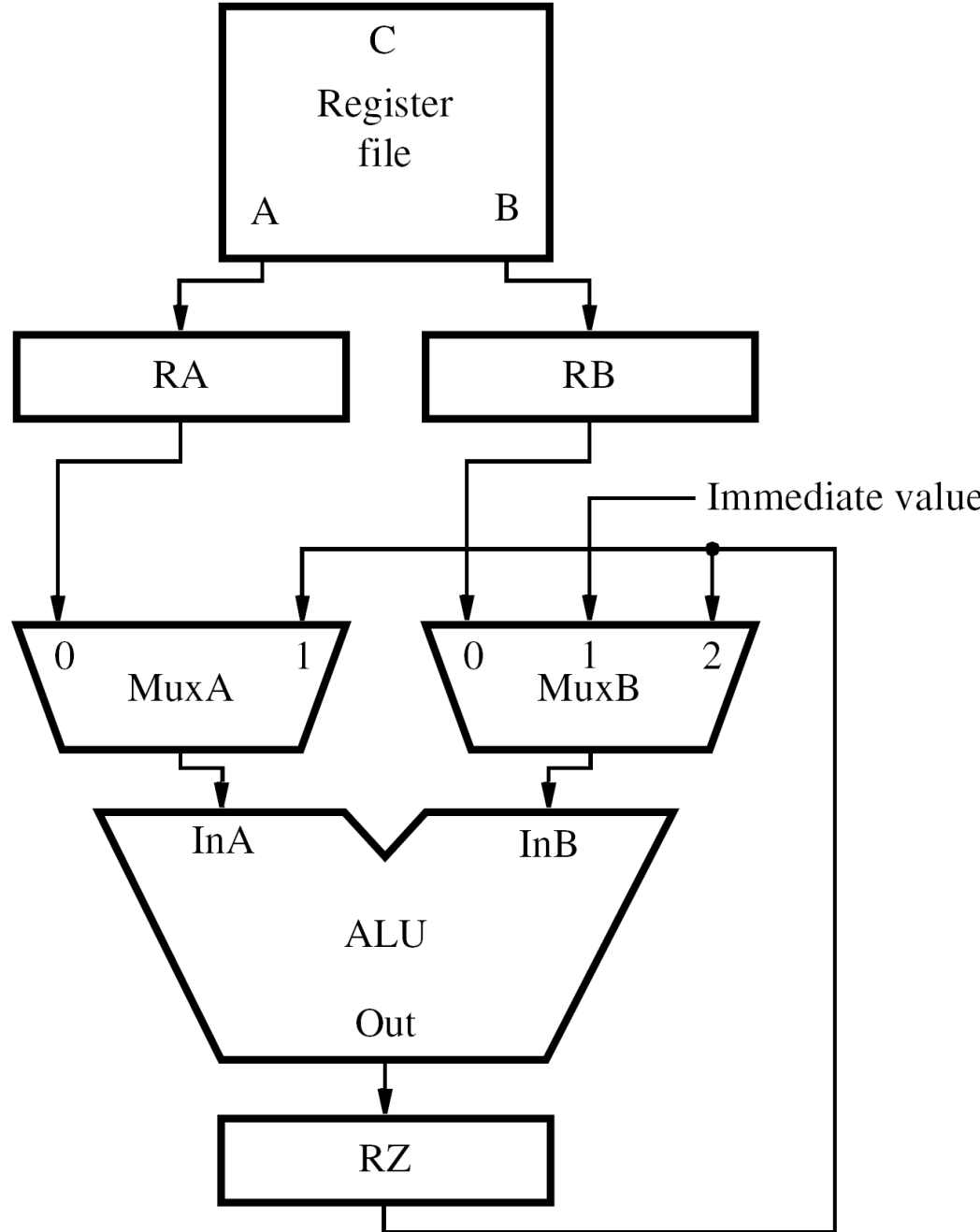Introduce multiplexers before ALU inputs to use contents of register RZ as forwarded value




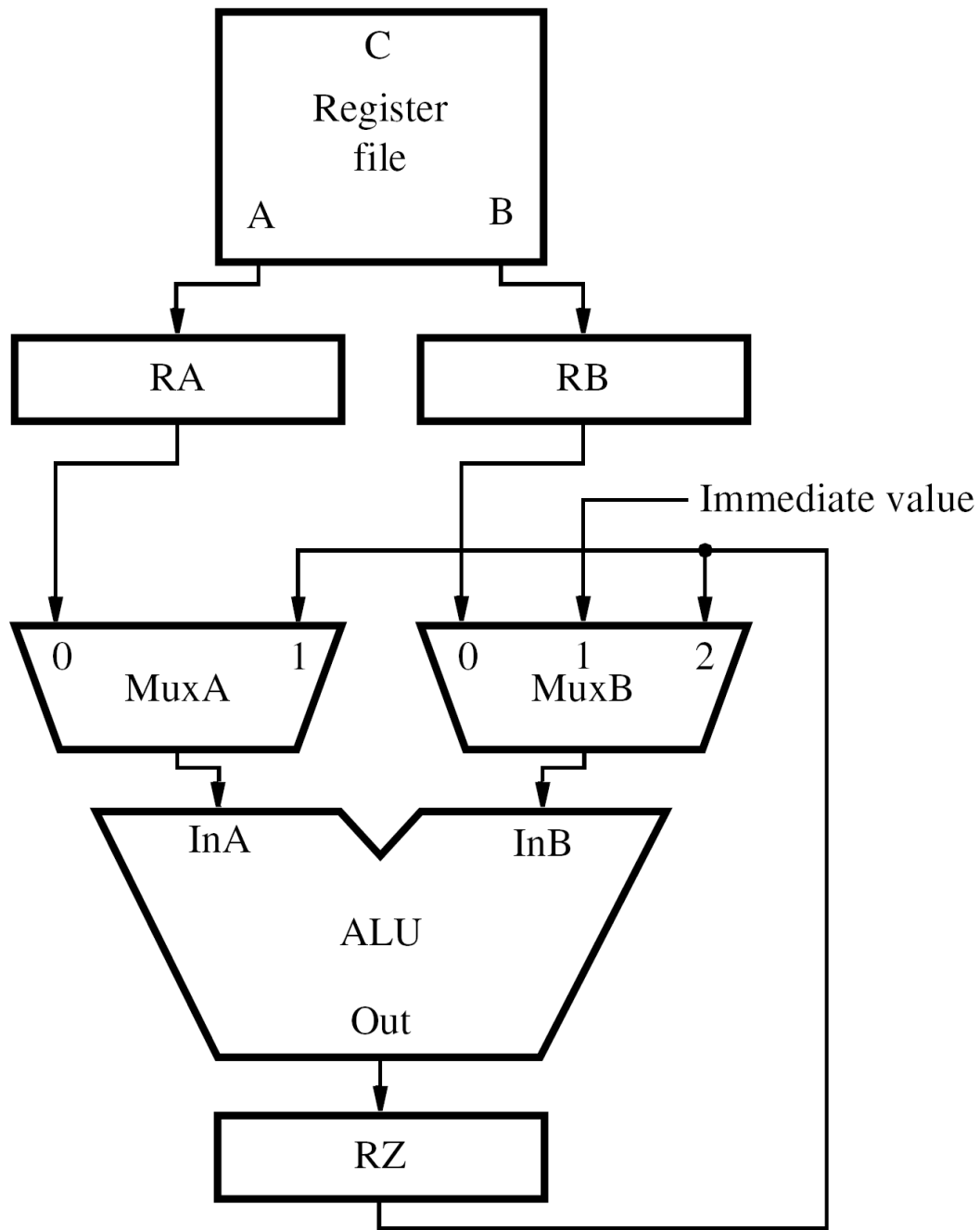


Another example of forwarding

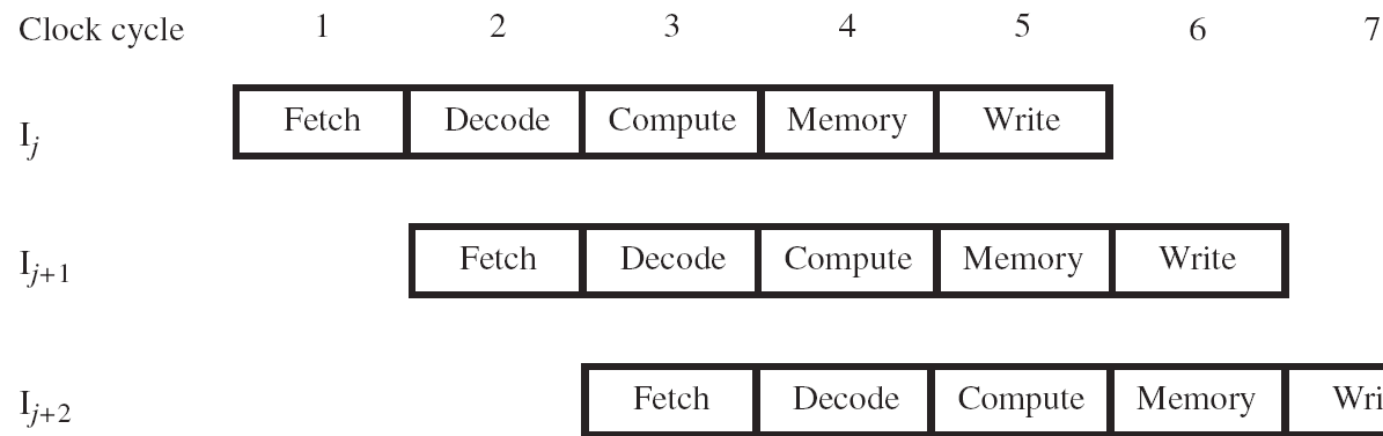

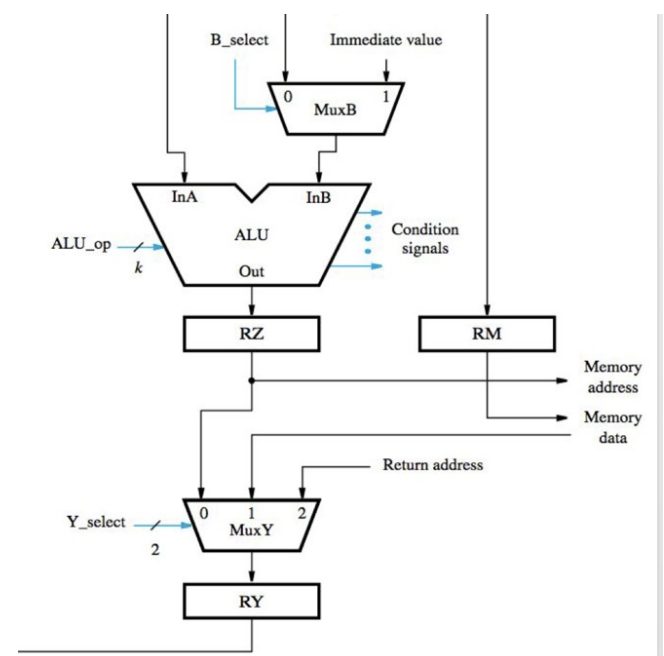I_j : ADD R2, R3, R7
 I_{j+1} : ORR R4, R5, R6
 I_{j+2} : SUB R9, R2, R8




Another example of forwarding

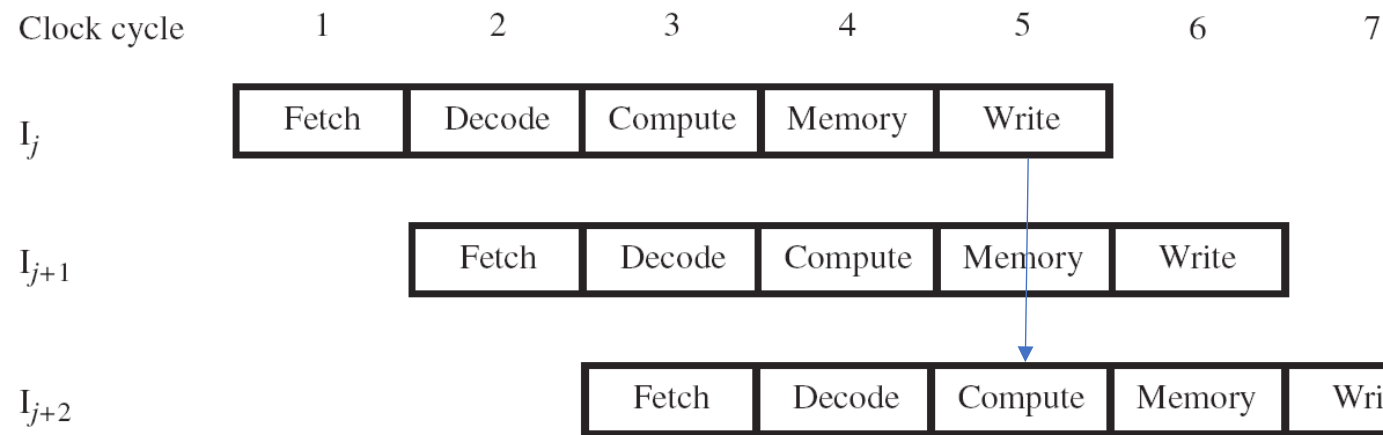


I_j : ADD R2, R3, R7
 I_{j+1} : ORR R4, R5, R6
 I_{j+2} : SUB R9, R2, R8

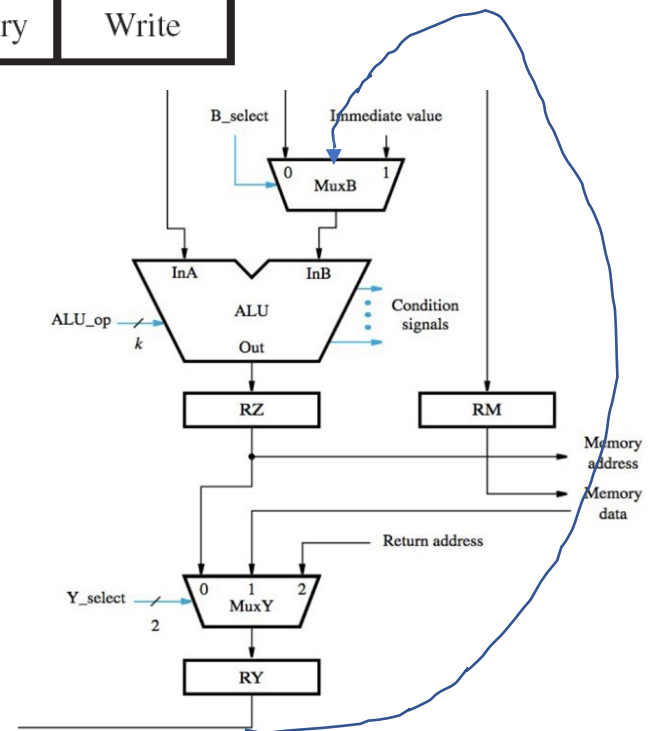Extend MuxB to allow forwarded input from RY




Software Handling of Dependencies

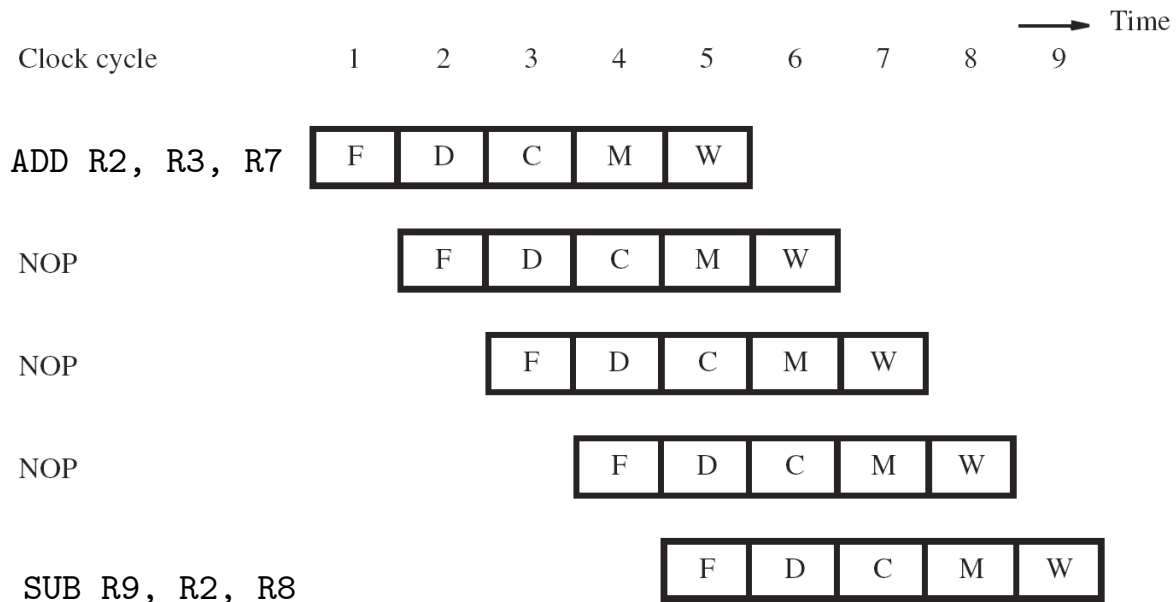- Data dependencies are evident at compile time
- Compiler puts three *explicit* NOP instructions between instructions having a dependency
- Delay ensures new value available in register but causes total execution time to increase
- Compiler can *optimize* by moving instructions into NOP slots (if data dependencies permit)




Memory delays

 

Cache misses result in delay in memory stage

Memory Delays

 
- Even with a cache *hit*, a Load instruction may cause a short delay due to a data dependency
- One-cycle stall required for correct value to be forwarded to instruction needing that value
- Optimize with useful instruction to fill delay



Branch Delays


- Ideal pipelining: fetch each new instruction while previous instruction is being decoded
- Branch instructions alter execution sequence – the branch instruction has to compute the target address and also perform a comparison to determine if we go to the target or fall-through instruction next
- Since these computations happen in later clock cycles, there is a hazard created when pipelining a branch instruction

Unconditional Branches

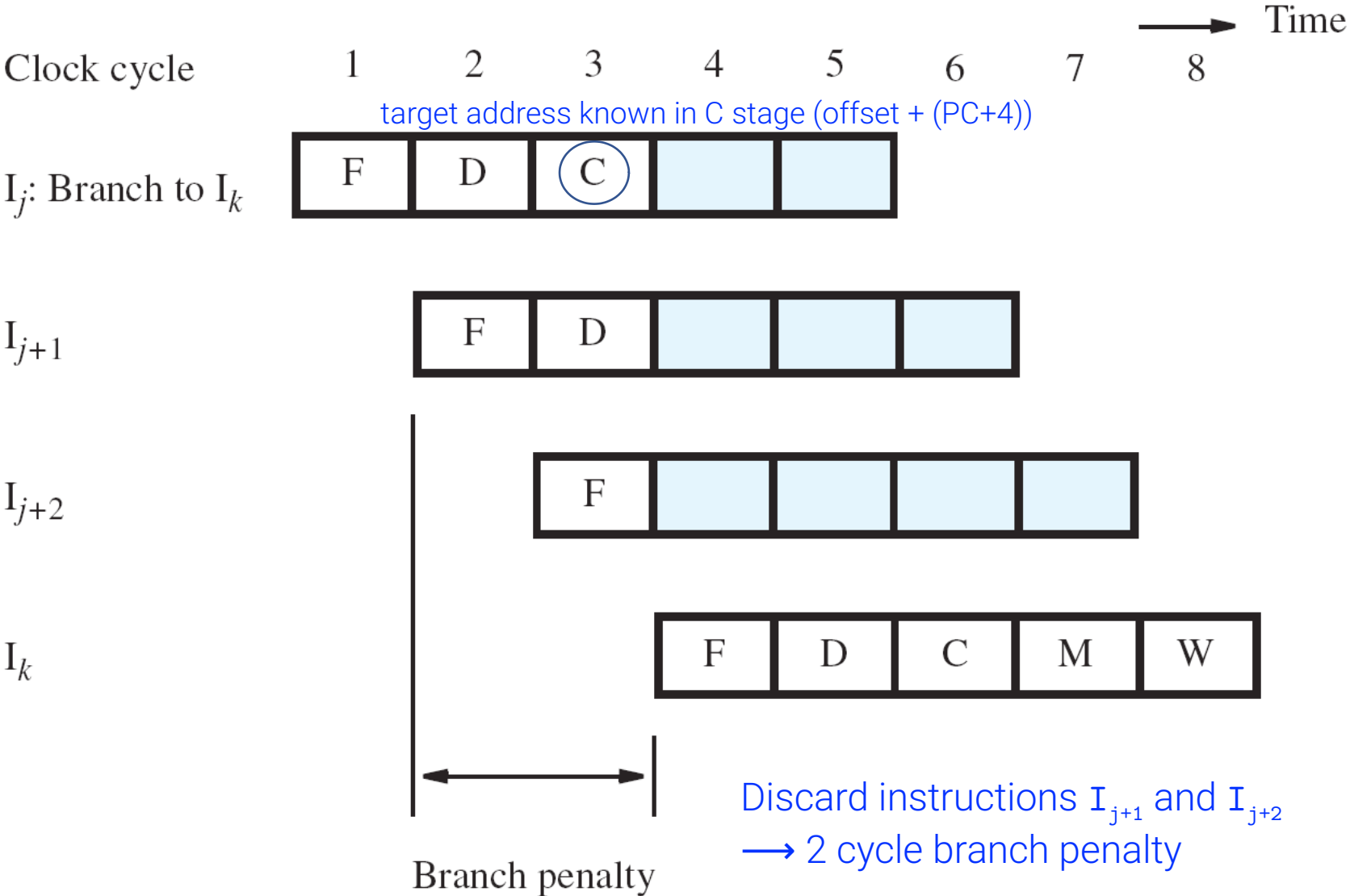

Reducing the Branch Penalty

 - Must compute the target address earlier in the pipeline
- Introduce a second adder dedicated to computing the branch target in the decode stage



Conditional Branches

```
BEQ R5, R6, LOOP
```

- Requires not only target address calculation, but also requires comparison in ALU for condition
- Target address now calculated in Decode stage (2 cycle penalty)
- How can we reduce to one-cycle penalty?
 - introduce a comparator just for branches in Decode stage

Delayed branching

- Assuming that both branch decision and target address are determined in Decode stage of pipeline, there is still an unavoidable branch delay of one cycle
- Allow the compiler to fill this *branch delay slot* with a useful instruction, usually from before the branch.
 - Alter the pipeline operation so that the Instruction immediately following a branch is *always* fetched and executed, regardless of branch decision
- If no suitable instruction can be found to fill the slot (because of dependencies) the compiler must put a NOP in the slot

Add	R7, R8, R9
Branch_if_[R3]=0	TARGET
I_{j+1}	
\vdots	
TARGET: I_k	

(a) Original sequence of instructions containing a conditional branch instruction

Branch_if_[R3]=0	TARGET
Add	R7, R8, R9
I_{j+1}	
\vdots	
TARGET: I_k	

(b) Placing the Add instruction in the branch delay slot where it is always executed

What's next

- In the next chapter we will look at how to efficiently do arithmetic in computers – how to build fast adders and multipliers for the compute stages in pipelines
- We will also learn about floating-point representation